

EXERCISE: What are the new W/L ratios for the transistors in Ex. 6.7 if $V_{TOL} = -1.5$ V?

ANSWERS: $(W/L)_S = 1.17/1$; $(W/L)_L = 1/1.72$

6.6.4 STATIC DESIGN OF THE PSEUDO NMOS INVERTER

It is also possible to replace the load resistor with a PMOS transistor with its source connected to V_{DD} , its drain is connected to the output node, and its gate connected to ground, as in Fig. 6.24. This circuit has become known as **pseudo NMOS** since circuit operation is very similar to that of NMOS logic even though it is usually found embedded in CMOS designs that we will study in detail in Chapter 7.

In order to design the circuit, we use the same circuit conditions that were used for the case of the resistive load. ($I_{DD} = 80$ μ A, $V_{DD} = 2.5$ V and $V_L = 0.20$ V). First we choose the W/L ratio of the PMOS load device to limit the operating current in the inverter. Then we calculate the size of M_S required to achieve the specified value of V_L . (Note that neither transistor suffers from any body effect since the bulk terminals of both transistors are connected to their respective sources. This is an important advantage of the PMOS load transistor in comparison to NMOS load devices.)

Calculation of $(W/L)_P$ and $(W/L)_S$

For the PMOS device in Fig. 6.24, we see that $V_{GS} = -V_{DD}$, and the transistor will be in the conducting state. Since $V_{DS} = 0.2 - 2.5 = -2.3$ V and $V_{GS} - V_{TP} = -2.5 - (-0.6) = -1.9$ V, the transistor will be saturated ($|V_{DS}| > |V_{GS} - V_{TP}|$ —see Section 4.2). We need to find the value of W/L that sets the PMOS drain current to 80 μ A:

$$i_D = \frac{K'_p}{2} \left(\frac{W}{L} \right)_p (V_{GS} - V_{TP})^2 \quad \text{or} \quad 80 \mu\text{A} = \frac{1}{2} \left(40 \frac{\mu\text{A}}{\text{V}^2} \right) \left(\frac{W}{L} \right)_p [-2.5 - (-0.6)]^2 \text{V}^2$$

$$\text{which gives } \left(\frac{W}{L} \right)_p = \frac{1.11}{1}.$$

Calculation of V_H and $(W/L)_S$

In order to calculate $(W/L)_S$, we need to determine the high output level V_H , since this is the voltage that is used to drive switching transistor M_S to achieve $v_O = V_L$. As shown in Fig. 6.24(b), the PMOS load transistor has a fixed value of $V_{GS} = -2.5$ V. Thus it will always be in the conducting state. With M_S off, current will flow through the PMOS device to charge the output node until the drain-source voltage V_{DS} of the transistor collapses to zero. Thus, $V_H = V_{DD}$, just as for the inverter with the resistor load.

Now, the conditions for switching transistor M_S with $v_O = V_L$ in Fig. 6.24(a) are $V_{GS} = V_H = 2.5$ V and $V_{DS} = V_L = 0.20$ V with $i_D = 80$ μ A. These are identical to those of the switching

 


Figure 6.24 Pseudo NMOS Inverter with (a) $v_I = V_H$ and (b) $v_I = V_L$.

 


Figure 6.25 Completed pseudo NMOS inverter design.

 


Figure 6.26 Pseudo NMOS inverter used in Ex. 6.8.

transistor in the resistor load inverter in Section 6.5.2. Thus, $(W/L)_S = 2.22/1$. The completed pseudo NMOS inverter design appears in Fig. 6.25.

EXERCISE: Verify the value of $(W/L)_S$ by calculating the drain current of M_S .

EXAMPLE 6.8 LOGIC LEVEL ANALYSIS FOR THE PSEUDO NMOS INVERTER

Finding the logic levels associated with someone else's inverter design involves a different thought process than that required to design the inverter. Here we find V_H and V_L for a specified inverter design.

PROBLEM Find the high and low logic levels and the power supply current for the pseudo NMOS inverter in Fig. 6.26 with $(W/L)_S = 10/1$ and $(W/L)_L = 2/1$. The inverter operates with $V_{DD} = 2.5$ V. Assume $K'_n = 100 \mu\text{A}/\text{V}^2$, $V_{TN} = 0.60$ V, $K'_p = 40 \mu\text{A}/\text{V}^2$, $V_{TP} = -0.60$ V.

SOLUTION **Known Information and Given Data:** Circuit topology in Fig. 6.26; $V_{DD} = 2.5$ V, $(W/L)_N = 10/1$, $(W/L)_P = 2/1$, $K'_n = 100 \mu\text{A}/\text{V}^2$, $V_{TN} = 0.60$ V, $K'_p = 40 \mu\text{A}/\text{V}^2$, and $V_{TP} = -0.60$ V.

Unknowns: V_H , V_L , I_{DD} for both logic states

Approach: First determine V_H . Use V_H and the specified transistor parameters to find V_L by equating the drain currents in the switching and load transistors. Use V_L to find power supply current I_{DD} which is equal to switching transistor drain current I_{DS} .

Assumptions: M_S is off for $v_I = V_L$. For $v_O = V_L$, M_S operates in the triode region, and M_L is in the saturation region.

Analysis: First we find V_H , and then we use it to find V_L . For the pseudo NMOS logic gate, $V_H = V_{DD}$. Thus, for our circuit, $V_H = 2.5$ V. To find V_L , we use the condition that the two transistor drain currents must be equal in the steady state: $I_{DS} = I_{DL}$. For $v_O = V_L$, we expect that the load transistor will be saturated since the magnitude of its drain-source voltage is large ($V_{DS} = V_L - V_{DD}$), and we expect the switching transistor to be in the triode region since its drain-source voltage will be small. ($V_{DS} = V_L$). For $I_{DS} = I_{DL}$, we have

$$K'_n \left(\frac{10}{1} \right) \left(V_{GSN} - V_{TN} - \frac{V_L}{2} \right) V_L = \frac{K'_p}{2} \left(\frac{2}{1} \right) (V_{GSP} - V_{TP})^2$$

For the circuit in Fig. 6.24, $V_{GSN} = 2.5$ V and $V_{GSP} = -2.5$ V, and

$$100 \frac{\mu\text{A}}{\text{V}^2} \left(\frac{10}{1} \right) \left(2.5 - 0.6 - \frac{V_L}{2} \right) V_L = \frac{40 \mu\text{A}}{2 \text{V}^2} \left(\frac{2}{1} \right) (-2.5 - (-0.6))^2$$

which can be rearranged to yield a quadratic equation:

$$12.5V_L^2 - 47.5V_L + 3.61 = 0 \quad \text{for which} \quad V_L = 0.0776 \text{ V}, \quad \cancel{3.72 \text{ V}}.$$


$V_L = 3.72 \text{ V}$ exceeds the 2.5-V power supply, so that answer must be discarded. Hence the answer must be $V_L = 0.0776 \text{ V}$. For this value of V_L , the current in M_S is

$$I_{DS} = \left(100 \frac{\mu\text{A}}{\text{V}^2}\right) \left(\frac{10}{1}\right) \left(2.5 - 0.6 - \frac{0.0776}{2}\right) (0.0776) \text{ V}^2 = 144 \mu\text{A}$$

Check of Results: For V_L , we should check our triode and saturation region assumptions for the two MOSFETs: For the switching transistor, $V_{GS} - V_{TN} = 2.5 - 0.6 = 1.90 \text{ V}$ which is greater than $V_{DS} = 0.078 \text{ V}$, and the triode region assumption is correct. For the load device, $V_{GS} - V_{TN} = -2.5 - (-0.6) = -1.9 \text{ V}$, and $V_{DS} = 0.078 - 2.5 = -2.42$, which are consistent with the saturation region of operation. We can further check our results by finding the drain current in M_L :

$$I_{DL} = \left(\frac{40 \mu\text{A}}{2 \text{ V}^2}\right) \left(\frac{2}{1}\right) (-2.5 + 0.6)^2 = 144 \mu\text{A} \quad \text{which agrees with } I_{DS}.$$

Computer-Aided Analysis: To verify our design with SPICE, we draw the circuit with a schematic capture tool. Two inverters are cascaded in order to get both V_H and V_L with one simulation. The gate of MS1 is grounded to force MS1 to be off. The NMOS transistor uses the LEVEL = 1 model with KP = 10E-5, VTO = 0.60 V, GAMMA = 0.5 and PHI = 0.6 V, and the PMOS parameters are KP = 4E-5, VTO = -0.60 V, GAMMA = 0.5 and PHI = 0.6 V. The transistor sizes are specified as W = 10 U and L = 1 U for M_S , and W = 2 U and L = 1 U for M_L . SPICE gives $V_H = 2.50 \text{ V}$ and $V_L = 0.0776 \text{ V}$. The current in V_{DD} is 144 μA . All the values agree with the hand calculations.

 

EXERCISE: Use the “Solver” in your calculator to check the value of V_L found in Section 6.7.2.

EXERCISE: Repeat the calculations with $(W/L)_S = 5/1$. Check your results with SPICE.

ANSWERS: 2.50 V, 0.159 V, 144 μA .

Noise Margin Analysis for the Pseudo NMOS Inverter

Let us now find the noise margins for the pseudo NMOS inverter. We need to calculate the values of V_{IL} , V_{OL} , V_{IH} , and V_{OH} and remember these voltages are defined by the points on the voltage transfer characteristic at which the slope $dv_O/dv_I = -1$, as indicated on the graph in Fig. 6.27.

First let us find V_{IL} and V_{OH} . We need to find a relationship between v_I and v_O that we can differentiate. Remember that the drain currents in the switching and load devices must be equal at all points on the static VTC. Also, at $v_I = V_{IL}$ the input will be at a relatively low voltage, and the

output will be a relatively high voltage. Thus, we guess that M_S will be operating in the saturation region and that M_L will operate in the triode region. Setting $i_{DS} = i_{DL}$ yields

$$\frac{K_S}{2}(v_I - V_{TN})^2 = K_L \left(-V_{DD} - V_{TP} - \frac{v_O - V_{DD}}{2} \right) (v_O - V_{DD}) \quad (6.29)$$

with

$$K_S = K'_n \left(\frac{W}{L} \right)_S \quad \text{and} \quad K_L = K'_p \left(\frac{W}{L} \right)_L$$

The point of interest is $\frac{\partial v_O}{\partial v_I} = -1$, but solving for the value of v_O would be quite tedious. Since we expect the derivatives to be smooth, continuous, and nonzero, we will assume that $\frac{\partial v_O}{\partial v_I} = \left(\frac{\partial v_I}{\partial v_O} \right)^{-1}$ and solve for v_I in terms of v_O :

$$v_I = V_{TN} + \frac{1}{\sqrt{K_R}} \sqrt{[2(V_{DD} + V_{TP}) - (V_{DD} - v_O)](V_{DD} - v_O)} \quad \text{where} \quad K_R = \frac{K_S}{K_L}$$

Evaluating the derivative is still quite tedious, so only the results are given here:⁶

$$V_{IL} = V_{TN} + \frac{(V_{DD} + V_{TP})}{\sqrt{K_R^2 + K_R}} \quad \text{and} \quad V_{OH} = V_{DD} - (V_{DD} + V_{TP}) \left(1 - \sqrt{\frac{K_R}{K_R + 1}} \right) \quad (6.30)$$

For the inverter design of Fig. 6.26 with $V_{DD} = 2.5$ V, $V_{TP} = -0.6$ V and $K_R = (2.22)(100)/(1.11)(40) = 5$, we find

$$V_{IL} = 0.6 + \frac{(2.5 - 0.6)}{\sqrt{(5)^2 + 5}} = 0.95 \text{ V} \quad \text{and} \quad V_{OH} = 2.5 - (2.5 - 0.6) \left(1 - \sqrt{\frac{5}{5 + 1}} \right) = 2.33 \text{ V}$$

These values appear reasonable. The input must exceed the threshold voltage of the NMOS transistor before it begins to conduct, so V_{IL} should be somewhat larger than V_{TN} , and the value of V_{OH} should be somewhat below V_{DD} as in Fig. 6.27.

With these values we can check our assumptions of the operating regions of M_S and M_L . For the NMOS switching transistor, $V_{GS} - V_{TN} = 0.95 - 0.6 = 0.35$ V and $V_{DS} = 2.33$ V. Since $V_{DS} > V_{GS} - V_{TN}$, the saturation region assumption was correct. For the PMOS load device, $V_{GS} - V_{TP} = -2.5 - (-0.6) = -1.9$ V and $V_{DS} = 2.33 - 2.5 = -0.17$ V. Since the magnitude of V_{DS} is less than that of $V_{GS} - V_{TP}$, the triode region assumption was correct.

A similar process is used to find V_{IH} and V_{OL} . We again observe that the drain currents in the switching and load devices must be equal. At $v_I = V_{IH}$, the input will be at a relatively high voltage, and the output will be at a relatively low voltage. Thus, we guess that M_S will operate in the triode region and M_L will be in the saturation region. Equating drain currents in the switching and load transistors yields

$$K_S \left(v_I - V_{TN} - \frac{v_O}{2} \right) v_O = \frac{K_L}{2} (-V_{DD} - V_{TP})^2 \quad (6.31)$$

We again assume that $\frac{\partial v_O}{\partial v_I} = \left(\frac{\partial v_I}{\partial v_O} \right)^{-1}$ and solve for v_I in terms of v_O :

$$v_I = V_{TN} + \frac{v_O}{2} + \frac{(V_{DD} + V_{TP})^2}{2K_R} \left(\frac{1}{v_O} \right) \quad \text{where} \quad K_R = \frac{K_S}{K_L} \quad (6.32)$$

⁶ The details of the derivation can be found on the MCD website.

 


Figure 6.27 PSPICE simulation of the voltage transfer function for the pseudo NMOS inverter.

 


Figure 6.28 Noise margins versus transconductance ratio K_R for the pseudo NMOS inverter with $V_{DD} = 2.5$ V, $V_{TN} = 0.6$ V and $V_{TP} = -0.6$ V.

Taking the derivative

$$\frac{\partial v_I}{\partial v_O} = \frac{1}{2} - \frac{1}{2K_R} \frac{(V_{DD} + V_{TP})^2}{v_O^2} \quad (6.33)$$

and setting it equal to -1 at $v_O = V_{OL}$ yields

$$-1 = \frac{1}{2} - \frac{1}{2K_R} \frac{(V_{DD} + V_{TP})^2}{V_{OL}^2} \quad \text{or} \quad V_{OL} = \frac{V_{DD} + V_{TP}}{\sqrt{3K_R}}$$

Substituting this result in Eq. (6.32) with $v_I = V_{IH}$ gives

$$V_{IH} = V_{TN} + \frac{2(V_{DD} + V_{TP})}{\sqrt{3K_R}} = V_{TN} + 2V_{OL} \quad (6.34)$$

For the inverter design of Fig. 6.26,

$$V_{OL} = \frac{V_{DD} + V_{TP}}{\sqrt{3K_R}} = \frac{(2.5 - 0.6) \text{ V}}{\sqrt{3(5)}} = 0.491 \text{ V} \quad \text{and} \quad V_{IH} = 0.6 + 2(0.49) = 1.58 \text{ V} \quad (6.35)$$

With these values we should again check our assumptions of the operating regions of M_S and M_L . For the NMOS switching transistor, $V_{GS} - V_{TN} = 1.58 - 0.6 = 0.98$ V and $V_{DS} = 0.491$ V. Since $V_{DS} < V_{GS} - V_{TN}$, the triode region assumption was correct. For the PMOS load device, $V_{GS} - V_{TP} = -2.5 - (-0.6) = -1.9$ V and $V_{DS} = 0.491 - 2.5 = -2.01$ V. Since the magnitude of V_{DS} exceeds that of $V_{GS} - V_{TP}$, the saturation region assumption was correct. In Fig. 6.27, it can be seen that these calculated values of V_{IL} , V_{OL} , V_{IH} and V_{OH} all agree well with SPICE simulation results.

The noise margins for this pseudo NMOS inverter are

$$NM_H = V_{OH} - V_{IH} = 2.33 - 1.58 = 0.75 \text{ V}$$

$$NM_L = V_{IL} - V_{OL} = 0.95 - 0.49 = 0.46 \text{ V}$$

With Eqs. (6.30)–(6.35), we can easily explore the dependence of the noise margins on transconductance ratio K_R , and the results are plotted in Fig. 6.28. High-state noise margin NM_H increases monotonically as the drive capacity of switching transistor M_S , and hence K_R , increases, whereas NM_L gradually decreases.

6.7 NMOS INVERTER SUMMARY AND COMPARISON

Figure 6.29 and Table 6.6 summarize the NMOS inverter designs discussed in Secs. 6.5 and 6.6. The gate with the resistive load takes up too much area to be implemented in IC form. The saturated load configuration is the simplest circuit, using only NMOS transistors. However, it has a disadvantage