

MICROELECTRONIC CIRCUIT DESIGN

Fourth Edition

Richard C. Jaeger and Travis N. Blalock

Answers to Selected Problems – Updated 2/27/11

Chapter 1

- 1.4 1.52 years, 5.06 years
- 1.5 1.95 years, 6.46 years
- 1.8 402 MW, 1.83 MA
- 1.10 2.50 mV, 5.12 V, 5.885 V
- 1.12 19.53 mV/bit, 10011000₂
- 1.14 14 bits, 20 bits
- 1.16 0.003 A, 0.003 cos (1000*t*) A
- 1.19 $v_{DS} = [5 + 2 \sin (2500t) + 4 \sin (1000t)]$ V
- 1.20 15.7 V, 2.32 V, 75.4 μA, 206 μA
- 1.22 150 μA, 150 μA, 12.3 V
- 1.24 39.8 Ω, 0.0251 v_s
- 1.27 56 kΩ, 1.60 x 10⁻³ v_s
- 1.29 1.50 MΩ, 7.50 x 10⁸ i_i
- 1.36 50/-12°, 10/-45°
- 1.38 -82.4 sin 750π*t* mV, 11.0 sin 750π*t* μA
- 1.40 1 + R₂/R₁
- 1.42 -1.875 V, -2.500 V
- 1.43 Band-pass amplifier
- 1.45 50.0 sin (2000π*t*) + 30.0 cos (8000 π*t*) V
- 1.48 0 V
- 1.47 [4653 Ω, 4747 Ω], [4465 Ω, 4935 Ω], [4230 Ω, 5170 Ω]
- 1.55 6200 Ω, 4.96 Ω/°C

1.61 3.29, 0.995, -6.16; 3.295, 0.9952, -6.155

Chapter 2

- 2.3 500 mA
- 2.4 160 Ω , 319 Ω
- 2.6 For Ge: $2.63 \times 10^{-4} / \text{cm}^3$, $2.27 \times 10^{13} / \text{cm}^3$, $8.04 \times 10^{15} / \text{cm}^3$,
- 2.9 305.2 K
- 2.10 $-1.75 \times 10^6 \text{ cm/s}$, $+6.25 \times 10^5 \text{ cm/s}$, $2.80 \times 10^4 \text{ A/cm}^2$, $1.00 \times 10^{-10} \text{ A/cm}^2$
- 2.11 $1.60 \times 10^6 \text{ A/cm}^2$, $1.60 \times 10^{-10} \text{ A/cm}^2$
- 2.13 4 MA/cm²
- 2.16 $1.60 \times 10^7 \text{ A/cm}^2$, 4.00 A
- 2.17 316.6 K
- 2.22 Donor, acceptor
- 2.23 200 V/cm
- 2.25 1.25×10^4 atoms
- 2.27 p-type, $6 \times 10^{18} / \text{cm}^3$, $16.7 / \text{cm}^3$, $5.28 \times 10^9 / \text{cm}^3$, $8.80 \times 10^{-10} / \text{cm}^3$
- 2.29 $3 \times 10^{17} / \text{cm}^3$, $333 / \text{cm}^3$
- 2.30 $4 \times 10^{16} / \text{cm}^3$, $2.50 \times 10^5 / \text{cm}^3$
- 2.34 $40 / \text{cm}^3$, $2.5 \times 10^{18} / \text{cm}^3$, $170 \text{ cm}^2 / \text{s}$, $80 \text{ cm}^2 / \text{s}$, p-type, 31.2 m Ω -cm
- 2.36 $10^{16} / \text{cm}^3$, $10^4 / \text{cm}^3$, $800 \text{ cm}^2 / \text{s}$, $220 \text{ cm}^2 / \text{s}$, n-type, 2.84 Ω -cm
- 2.38 $1.16 \times 10^{20} / \text{cm}^3$
- 2.40 $1.24 \times 10^{19} / \text{cm}^3$
- 2.41 Yes—add equal amounts of donor and acceptor impurities. Then $n = n_i = p$, but the mobilities are reduced. See Prob. 2.44.
- 2.43 $6.27 \times 10^{21} / \text{cm}^3$, $6.22 \times 10^{21} / \text{cm}^3$
- 2.46 2.00/ Ω -cm, $2.50 \times 10^{19} / \text{cm}^3$
- 2.48 75K: 6.64 mV, 150K: 12.9 mV, 300K: 25.8 mV, 400K: 34.5 mV
- 2.49 -28.0 kA/cm²
- 2.50 $1.20 \times 10^5 \exp(-5000 \text{ x/cm}) \text{ A/cm}^2$, 12.0 mA
- 2.54 1.108 μm
- 2.57 8 atoms, $1.60 \times 10^{-22} \text{ cm}^3$, $5.00 \times 10^{22} \text{ atoms/cm}^3$, $3.73 \times 10^{-23} \text{ g}$, $1.66 \times 10^{-24} \text{ g/proton}$

Chapter 3

- 3.1 0.0373 μm , 0.0339 μm , $3.39 \times 10^{-3} \mu\text{m}$, 0.979 V, $5.24 \times 10^5 \text{ V/cm}$
- 3.4 $10^{18}/\text{cm}^3$, $10^2/\text{cm}^3$, $10^{18}/\text{cm}^3$, $10^2/\text{cm}^3$, 0.921 V, 0.0488 μm
- 3.6 6.80 V, 1.22 μm
- 3.10 640 kA/cm^2
- 3.13 $1.00 \times 10^{21}/\text{cm}^4$
- 3.17 290 K
- 3.20 312 K
- 3.21 1.39, 3.17 pA
- 3.22 0.791 V; 0.721 V; 0 A; 9.39 aA, -10.0 aA
- 3.25 1.34 V; 1.38 V
- 3.28 0.518 V; 0.633 V
- 3.29 335.80 K, 296.35 K
- 3.33 0.757 V; 0.717 V
- 3.35 -1.96 mV/K
- 3.39 0.633 V, 0.949 μm , 3.89 μm , 12.0 μm
- 3.40 374 V
- 3.42 4 V, 0 Ω
- 3.44 10.5 nF/cm²; 232 pF
- 3.46 800 fF, 20 fC; 20 pF, 0.5 pC
- 3.50 9.87 MHz; 15.5 MHz
- 3.51 0.495 V, 0.668 V
- 3.53 0.708 V, 0.718 V; 0.808 V
- 3.58 (a) Load line: (450 μA , 0.500 V); SPICE: (443 μA , 0.575 V)
(b) Load line: (-667 μA , -4 V);
(c) Load line: (0 μA , -3 V);
- 3.61 (0.600 mA, -4 V) , (0.950 mA, 0.5 V) , (-2.00 mA, -4 V)
- 3.68 Load line: (50 μA , 0.5 V); Mathematical model: (49.9 μA , 0.501 V); Ideal diode model: (100 μA , 0 V); CVD model: (40.0 μA , 0.6 V)
- 3.72 (a) 0.625 mA, -5 V; 0.625 mA, +3 V; 0 A, 7 V; 0 A, -5 V

- 3.74 (c) (270 μA , 0 V), (409 μA , 0 V); (c) (0 A -3.92 V), (230 μA , 0 V)
- 3.76 (b) (0.990 mA, 0 V) (0 mA, -1.73 V) (1.09 mA, 0)
(c) (0 A, -0.667 V) (0 A, -1.33 V) (1.21 mA, 0 V)
- 3.79 (1.50 mA, 0 V) (0 A, -5.00 V) (1.00 mA, 0)
- 3.82 (I_Z , V_Z) = (887 μA , 4.00 V)
- 3.84 12.6 mW
- 3.86 1.25 W, 3.50 W
- 3.91 17.6 V
- 3.95 -7.91 V, 1.05 F, 17.8 V, 3530 A, 840 A ($\Delta T = 0.628$ ms)
- 3.97 (b) -7.91V, 904 μF , 17.8 V, 3540 A, 839 A
- 3.99 6.06 F, 8.6 V, 3.04 V, 962 A, 9280 A
- 3.104 -24.5 V, 1.63 F, 50.1 V, 15600 A, 2200 A
- 3.107 3.03 F, 8.6 V, 3.04 V, 962 A, 3770 A
- 3.112 2380 μF , 2800 V, 1980 V, 126 A, 2510 A
- 3.119 5 mA, 4.4 mA, 3.6 mA, 5.59 ns
- 3.123 (0.969 A, 0.777 V); 0.753 W; 1 A, 0.864 V
- 3.125 1.11 μm , 0.875 μm ; far infrared, near infrared

Chapter 4

- 4.3 $10.5 \times 10^{-9} \text{ F/cm}^2$
- 4.4 $43.2 \mu\text{A/V}^2$, $86.4 \mu\text{A/V}^2$, $173 \mu\text{A/V}^2$, $346 \mu\text{A/V}^2$
- 4.8 (a) 4.00 mA/V^2 (b) 4.00 mA/V^2 , 8.00 mA/V^2
- 4.11 $+840 \mu\text{A}$; $-880 \mu\text{A}$
- 4.15 23.0Ω ; 50.0Ω
- 4.18 $125 \mu\text{A/V}^2$; 1.5 V ; enhancement mode; 1.25/1
- 4.20 0 A , 0 A , 1.88 mA , 7.50 mA , 3.75 mA/V^2
- 4.22 1.56 mA , saturation region; $460 \mu\text{A}$, triode region; 0 A , cutoff
- 4.23 saturation; cutoff; saturation; triode; triode; triode
- 4.27 6.50 mS , 13.0 mS
- 4.30 2.48 mA ; 2.25 mA
- 4.34 9.03 mA , 18.1 mA , 10.8 mA
- 4.37 1.13 mA ; 1.29 mA
- 4.39 Triode region
- 4.40 $99.5 \mu\text{A}$; $199 \mu\text{A}$; $99.5 \mu\text{A}$; $99.5 \mu\text{A}$
- 4.44 $202 \mu\text{A}$; $184 \mu\text{A}$
- 4.46 5.17 V
- 4.51 $40.0 \mu\text{A}$; $72.0 \mu\text{A}$; $4.41 \mu\text{A}$; $32.8 \mu\text{A}$
- 4.53 5810/1; 2330/1
- 4.56 235Ω ; 235Ω
- 4.57 0.629 A/V^2
- 4.58 $400 \mu\text{A}$
- 4.61 The transistor must be a depletion-mode device and the symbol is not correct.
- 4.65 (a) $6.09 \times 10^{-8} \text{ F/cm}^2$; 1.73 fF
- 4.67 17.3 pF/cm
- 4.69 20.7 nF
- 4.71 (a) 1.35 fF , 0.20 fF , 0.20 fF
- 4.74 50U, 0.5U, 2.5U, 1V, 0
- 4.77 10U, 0.5U, 25U, 1V, 0

- 4.79 $432 \mu\text{A}/\text{V}^2$, 1.94 mA; $864 \mu\text{A}/\text{V}^2$, 0.972 mA
- 4.82 6.37 GHz, 2.55 GHz; 637 GHz, 255 GHz
- 4.85 $22\lambda \times 12\lambda$; 15.2%
- 4.88 $12\lambda \times 12\lambda$; 15.2%
- 4.89 (350 μA , 1.7 V); triode region
- 4.92 (390 μA , 4.1 V); saturation region
- 4.95 (572 μA , 7.94 V); (688 μA , 7.52 V)
- 4.97 (50.3 μA , 8.43 V) ; (54.1 μA , 8.16 V)
- 4.102 (a) (116 μA , 4.15 V)
- 4.105 510 k Ω , 470 k Ω , 12 k Ω , 12 k Ω , 5/1
- 4.107 (124 μA , 2.36 V)
- 4.109 620 k Ω , 910 k Ω , 2.4 k Ω , 2.7 k Ω
- 4.111 (109 μA , 1.08 V); (33.5 μA , 0.933 V)
- 4.113 (42.6 μA , 0.957 V); (42.6 μA , 0.935 V)
- 4.115 8.8043×10^{-5} A; 8.323310^{-5} A
- 4.118 (73.1 μA , 9.37 V)
- 4.119 (69.7 μA , 9.49 V); (73.1 μA , 8.49 V)
- 4.122 (8.17 μA , 7.06 V), (6.74 μA , 7.57 V); (8.36 μA , 6.99 V), (6.89 μA , 7.52 V)
- 4.124 (91.5 μA , 8.70 V), (70.7 μA , 9.23 V); (97.8 μA , 8.48 V), (81.9 μA , 9.05 V)
- 4.125 2.25 mA; 16.0 mA; 1.61 mA
- 4.127 (322 μA , 3.18 V),
- 4.129 18.1 mA; 45.2 mA; 13.0 mA
- 4.131 1/3.84
- 4.132 (153 μA , -3.53 V) ; (195 μA , -0.347 V)
- 4.134 4.04 V, 10.8 mA; 43.2 mA; 24.5 mA; 98.0 mA
- 4.135 14.4 mA; 27.1 mA; 10.4 mA
- 4.137 (1.13 mA, 1.75 V)
- 4.138 (63.5 μA , -5.48 V) , $R \leq 130 \text{ k}\Omega$
- 4.140 (55.3 μA , -7.09 V) , $R \leq 164 \text{ k}\Omega$
- 4.143 $22.3 \text{ k}\Omega \rightarrow (127 \mu\text{A}, -5.50 \text{ V})$

- 4.146** $35.2 \mu\text{A}$, $R \leq 318 \text{ k}\Omega$
- 4.148** One possible design: $220 \text{ k}\Omega$, $200 \text{ k}\Omega$, $5.1 \text{ k}\Omega$, $4.7 \text{ k}\Omega$
- 4.149** ($281 \mu\text{A}$, -12.2 V)
- 4.151** ($32.1 \mu\text{A}$, -1.41 V)
- 4.153** ($36.1 \mu\text{A}$, 80.6 mV); ($32.4 \mu\text{A}$, -1.32 V); ($28.8 \mu\text{A}$, -2.49 V)
- 4.155** ($431 \mu\text{A}$, 6.47 V)
- 4.156** $2.5 \text{ k}\Omega$, $10 \text{ k}\Omega$
- 4.157** $I_D = 1.38 \text{ mA}$, $I_G = 0.62 \text{ mA}$, $V_S = -0.7 \text{ V}$
- 4.159** ($76.4 \mu\text{A}$, 7.69 V), ($76.4 \mu\text{A}$, 6.55 V), 5.18 V
- 4.160** (a) ($69.5 \mu\text{A}$, 3.52 V)
- 4.162** ($69.5 \mu\text{A}$, 5.05 V); ($456 \mu\text{A}$, 6.20 V),
- 4.167** 10.0 V ; 10.0 mA , 501 mA ; 13.8 V
- 4.169** 15.0 V ; 15.0 mA , 1.00 A ; 12.2 V

Chapter 5

- 5.4 0.167, 0.667, 3.00, 0.909, 49.0, 0.995, 0.999, 5000
- 5.5 0.2 fA; 0.101 fA, -0.115 V
- 5.6 0.374 μ A, -149.6 μ A, +150 μ A, 0.626 V
- 5.9 0.404 fA
- 5.11 1.45 mA; -1.45 mA
- 5.14 -25 μ A, -100 μ A, +75 μ A, 65.7, 1/3, 0, 0.599 V
- 5.17 1.77 μ A, -33.2 μ A, +35 μ A, 0.623 V
- 5.20 (a) 723 μ A
- 5.24 0.990, 0.333, 2.02 fA, 6.00 fA
- 5.26 83.3, 87.5, 100
- 5.33 39.6 mV/dec, 49.5 mV/dec, 59.4 mV/dec, 69.3 mV/dec
- 5.34 5 V, 60 V, 5 V
- 5.35 2.31 mA; 388 μ A; 0
- 5.36 60.7 V
- 5.40 Cutoff
- 5.42 saturation, forward-active region, reverse-active region, cutoff
- 5.46 25.0 aA, 1.33 aA, 26.3 aA
- 5.47 $I_C = 81.4$ pA, $I_E = 81.4$ pA, $I_B = 4.28$ pA, forward-active region; although I_C , I_E , I_B are all very small, the Transport model still yields $I_C \cong \beta_F I_B$
- 5.48 79.0, 6.83 fA
- 5.49 83.3, 1.73 fA
- 5.50 55.3 μ A, 0.683 μ A, 54.6 μ A
- 5.51 6.67 MHz; 500 MHz
- 5.53 1.5, 31.1 aA
- 5.55 -19.9 μ A, 26.5 μ A, -46.4 μ A
- 5.58 17.3 mV, 0.251 mV
- 5.60 1.81 A, 10.1 A
- 5.62 0.768 V, 0.680 V, 27.5 mV
- 5.65 24.2 μ A
- 5.66 4.0 fF; 0.4 pF; 40 pF

- 5.68** 750 MHz, 3.75 MHz
- 5.71** 0.149 μm
- 5.72** 71.7, 43.1 V
- 5.74** 74.1, 40.0 V
- 5.75** 100 μA , 4.52 μA , 95.5 μA , 0.651 V, 0.724
- 5.77** 26.3 μA
- 5.78** (c) 33.1 mS
- 5.79** 0.388 pF at 1 mA
- 5.81** (b) 38% reduction
- 5.83** (80.9 μA , 3.80 V) ; (405 μA , 3.80 V); (16.2 μA , 3.80 V) ; (81.9 μA , 3.72 V);
- 5.88** (38.8 μA , 5.24 V)
- 5.90** 36 k Ω , 75 k Ω , 3.9 k Ω , 3 k Ω ; (0.975 mA, 5.24 V)
- 5.93** 12 k Ω , 20 k Ω , 2.4 k Ω , 1.2 k Ω ; (0.870 mA, 1.85 V)
- 5.95** (7.5 mA, 4.3 V)
- 5.97** (5.0 mA, 1.3 V)
- 5.99** 30 k Ω , 620 k Ω ; 24.2 μA , 0.770 V
- 5.101** 5.28 V
- 5.103** 3.21 Ω
- 5.104** 10 V, 100 mA, 98.5 mA, 10.7 V
- 5.105** 10 V, 109 mA, 109 mA, 14.3 V

Chapter 6

- 6.1 $10 \mu\text{W}/\text{gate}$, $8 \mu\text{A}/\text{gate}$
- 6.3 2.5 V , 0 V , 0 W , $62.5 \mu\text{W}$; 3.3 V , 0 V , 0 V , $109 \mu\text{W}$
- 6.5 $V_{OL} = 0 \text{ V}$, $V_{OH} = 2.5 \text{ V}$, $V_{REF} = 0.8 \text{ V}$; $Z = A$
- 6.7 3 V , 0 V , 2 V , 1 V , -3
- 6.9 2 V , 0 V , 2 V , 5 V , 3 V , 2 V
- 6.11 3.3 V , 0 V , 3.0 V , 0.25 V , 1.8 V , 1.5 V , 1.2 V , 1.25 V
- 6.13 -0.80 V , -1.35 V
- 6.15 1 ns
- 6.17 $0.152 \mu\text{W}/\text{gate}$, 22.7 aJ
- 6.19 $2.5 \mu\text{W}/\text{gate}$, $1.39 \mu\text{A}/\text{gate}$, 2.5 fJ
- 6.20 $2.20 RC$; $2.20 RC$
- 6.22 -0.78 V , -1.36 V ; 9.5 ns , 9.5 ns ; 4 ns , 4 ns ; 4 ns
- 6.25 $Z = 0 1 0 1 0 1 0 1$
- 6.27 $Z = 0 0 0 1 0 0 1 1$
- 6.30 $2 ; 1$
- 6.32 84.5 A
- 6.33 0.583 pF
- 6.37 $3 \mu\text{W}/\text{gate}$, $1.67 \mu\text{A}/\text{gate}$
- 6.38 $72 \text{ k}\Omega$, $1/1.04$
- 6.39 (b) 2.5 V , 5.48 mV , $15.6 \mu\text{W}$
- 6.43 (a) 0.450 V , 1.57 V
- 6.46 (a) 0.521 V , 1.81 V
- 6.49 NM_L : 0.242 V , 0.134 V , 0.351 V ; NM_H : 0.941 V , 0.508 V , 1.25 V
- 6.51 $34.1 \text{ k}\Omega$; $1.82/1$; 1.49 V , 0.266 V
- 6.53 $81.8 \text{ k}\Omega$, $1/1.15$
- 6.54 250Ω ; 625Ω ; a resistive channel exists connecting the source and drain; $20/1$
- 6.55 1.44 V
- 6.57 2.17 V
- 6.58 1.55 V , 0.20 V , 0.140 mW , 0.260 mW

- 6.62 2.5 V, 0.206 V, 0.434 mW
- 6.65 1.40/1, 6.67/1
- 6.67 (b) 2.43/1, 1/3.97
- 6.69 0.106 V
- 6.71 1.55 V, 0.20 V, 0.150 mW
- 6.74 -2.40 at $v_O = 0.883$ V
- 6.75 -2.44 at $v_O = 1.08$ V
- 6.77 3.79 V
- 6.79 3.3 V, 0.296 V, 1.25 mW
- 6.82 1.75/1, 1/8.79
- 6.84 1.014
- 6.85 1.46/1, 1.72/1
- 6.86 2.5 V, 0.2 V, 0.16 mW
- 6.89 -5.98 at $v_O = 1.24$ V
- 6.90 1.80/1, 0.610 V, 0.475 V
- 6.91 (a) 0.165 V, 80 μ A (b) 0.860 V, 0.445 V
- 6.93 (a) 0.224 V, 88.8 μ A (b) 0.700 V, 0.449 V
- 6.95 1.65/1, 1/2.32, 0.300 V, 0.426 V
- 6.97 0.103 V, 84.5 μ A
- 6.98 0.196 V
- 6.102 2.22/1, 1.81/1
- 6.103 2.22/1, 1.11/1, 0.0643 V
- 6.104 6.66/1, 1.11/1, 0.203 V, 6.43/1, 6.74/1, 7.09/1
- 6.107 $Y = \overline{(A+B)(C+D)E}$, 6.66/1, 1.11/1
- 6.111 $Y = \overline{ACE + ACDF + BF + BDE}$, 3.33/1, 26.6/1, 17.8/1
- 6.115 1/1.80, 3.33/1
- 6.117 $Y = \overline{(C+E)[A(B+D)+G]+F}$; 3.62/1, 13.3/1, 4.44/1, 6.67/1
- 6.120 3.45/1, 6.43/1, 7.09/1, 6.74/1
- 6.122 1.11/1, 7.09/1, 6.43/1, 6.74/1
- 6.124 64.9 mV

- 6.126** (a) 5.43/1, 9.99/1, 6.66./1, 20.0/1
- 6.128** (a) 7.24/1, 26.6/1, 13.3/1
- 6.132** $I_D^* = 2I_D$ | $P_D^* = 2P_D$
- 6.133** 80 mW, 139 mW
- 6.134** 1 ns
- 6.137** 60.2 ns, a potentially stable state exists with no oscillation
- 6.139** 31.7 ns, 4.39 ns, 5.86 ns
- 6.141** 5.50 k Ω , 11.6/1
- 6.144** 68,4 ns, 3.55 ns, 9.18 ns
- 6.146** 47.1 ns, 6.14 ns, 5.39 ns
- 6.148** 2.11/1, 16.7/1, 12.8 ns, 0.923 ns
- 6.149** 2.68/1, 3.29/1, 884 μ W
- 6.150** (a) 1/1.68 (d) 1/5.89 (f) 1/1.60
- 6.152** -1.90 V, -0.156 V
- 6.153** 1/3.30, 1.75/1
- 6.154** 2.30 V, 1.07 V
- 6.156** $Y = \overline{A + B}$

Chapter 7

- 7.1 $173 \mu\text{A}/\text{V}^2$; $69.1 \mu\text{A}/\text{V}^2$
- 7.3 250 pA; 450 pA; 450 pA
- 7.6 2.5 V, 0 V
- 7.8 cutoff, triode, triode, cutoff, saturation, saturation
- 7.11 1.25 V; 42.3 μA ; 1.104 V; 25.4 μA
- 7.12 0.90 V; 16.0 μA ; 0.810 V; 96.2 μA
- 7.14 1.104 V
- 7.15 (b) 2.5 V, 92.8 mV
- 7.17 1.16 V, 0.728 V
- 7.18 0.810 V
- 7.22 0.9836 V, 2.77 mA
- 7.23 6.10/1, 1/5.37
- 7.24 (a) 1.89 ns, 1.89 ns, 0.630 ns
- 7.27 9.47 ns, 3.97 ns, 2.21 ns
- 7.31 2.11/1, 5.26/1
- 7.33 63.2/1, 158/1
- 7.35 6.00/1, 15.0/1
- 7.38 2.76/1
- 7.41 1.7 ns, 2.3 ns, 1.1 ns, 0.9 ns, $\langle C \rangle = 138 \text{ fF}$
- 7.43 0.200 $\mu\text{W}/\text{gate}$; 55.6 A
- 7.44 1.0 $\mu\text{W}/\text{gate}$; 18.4 fF; 32.0 fF; 61.7 fF
- 7.46 5.00 W; 8.71 W
- 7.49 90.3 μA ; 25.0 μA
- 7.52 436 fJ; 425 MHz; 926 μW
- 7.55 $\alpha\Delta T$, $\alpha^2 P$, $\alpha^3 \text{PDP}$
- 7.58 SPICE: 22.3 ns, 24.2 ns, 16.3 ns, 18.3 ns; Propagation delay formulas: 7.6 ns, 6.9 ns
- 7.59 2/1, 20/1; 6/1, 60/1
- 7.61 1/3.75
- 7.63 1.25/1

- 7.70 3.95 ns, 3.95 ns, 11.8 ns
- 7.71 4.67/1; 7.5/1
- 7.72 5 transistors; The CMOS design requires 47% less area.
- 7.74 $Y = \overline{(A+B)(C+D)}E = \overline{ACE + ADE + BDE + BCE}$; 12/1, 20/1, 10/1; 2.4/1; 30/1
- 7.76 $Y = \overline{(\overline{A+B})(\overline{C+D})(\overline{E+F})} = \overline{AB + CD + EF}$; 4/1, 15/1; 6/1; 10/1
- 7.78 2/1, 4/1, 6/1, 20/1
- 7.81 (a) Path through NMOS A-D-E (d) Paths through PMOS A-C and B-E
- 7.83 24/1, 20/1, 40/1
- 7.84 6/1, 4/1, 10/1
- 7.91 5.37 ns, 1.26 ns
- 7.93 1.26 ns, 0.737 ns, 4.74 ns, 4.16 ns
- 7.95 4.74 ns, 2.37 ns
- 7.103 $V_{DD} \rightarrow \frac{2}{3}V_{DD} \rightarrow \frac{1}{2}V_{DD}$; $R \geq \frac{2V_{IH}}{V_{DD} - V_{IH}} = \frac{2V_{IH}}{NM_H}$, $C_1 \geq 83.1C_2$
- 7.109 8; 2.90; 23.2 A_o
- 7.112 $A_o \frac{\beta^N - 1}{\beta - 1}$
- 7.113 263 Ω; 658 Ω
- 7.116 240/1, 96.2/1
- 7.117 1.41 V, 2.50 V
- 7.119 Latchup does not occur.
- 7.122 +0.25; +0.31
- 7.124 211,000/1; 0.0106 cm²

Chapter 8

- 8.1** 268,435,456 bits, 1,073,741,824 bits; 2048 blocks
- 8.2** 3.73 pA/cell , 233 fA/cell
- 8.5** 3 V, 0.667 μ V
- 8.9** 1.55 V, 0 V, 3.59 V
- 8.11** “1” level is discharged by junction leakage current
- 8.13** 1.47 V, 1.43 V
- 8.14** -19.8 mV; 2.48 V
- 8.16** 0 V, 1.90; Junction leakage will destroy the “1” level
- 8.18** 5.00 V, 1.60 V; -1.84 V
- 8.22** 135 μ A, 346 mW
- 8.24** 0.266 V
- 8.25** 0.945 V (The sense amplifier provides a gain of 10.5.)
- 8.31** 0 V, 1.43 V, 3.00 V
- 8.32** 0.8 V, 1.2 V; 0.95 V, 0.95 V
- 8.34** 53,296
- 8.37** $V_{DD} \rightarrow \frac{2}{3}V_{DD} \rightarrow \frac{1}{2}V_{DD}$; $R \geq \frac{2V_{IH}}{V_{DD} - V_{IH}} = \frac{2V_{IH}}{NM_H}$; $C_1 \geq 2.88C_2$
- 8.41** $W_1 = 01000110_2$, $W_3 = 00101011_2$
- 8.45** 1.16/1

Chapter 9

- 9.1 0 V, -0.700 V
- 9.2 (a) -1.38 V, -1.12
- 9.3 -1.50 V, 0 V
- 9.6 0 V, -0.40 V; 3.39 k Ω ; Saturation, cutoff; Cutoff, saturation
- 9.8 -0.70 V, -1.30 V, -1.00 V, 0.60 V
- 9.11 -0.70 V, -1.50 V, -1.10 V, 2.67 k Ω ; 0.289 V; -0.10 V, +0.30 V
- 9.13 -1.70 V, -2.30 V, 0.60 V, Yes
- 9.15 11
- 9.16 11.1 k Ω , 12.0 k Ω , 70.2 k Ω , 252 k Ω
- 9.18 -1.10 V, -1.50 V, -1.30 V, 0.400 V, 0.107 V, 1.10 mW
- 9.19 0.383 V
- 9.21 -0.70 V, -1.50 V, -1.10 V, 11.3 k Ω , 2.67 k Ω , 2.38 k Ω ; 0.289 V
- 9.23 0.413 V
- 9.25 50.0 μ A, -2.30 V
- 9.26 Standard values: 11 k Ω , 150 k Ω , 136 k Ω
- 9.30 +0.300 V, -0.535 V, 334 Ω
- 9.33 5.15 mA
- 9.36 0.135 mA
- 9.38 10.7 mA
- 9.40 400 Ω , 75.0 mA
- 9.42 (c) 0 V, -0.7 V, 3.93 mA (d) -3.7 V, 0.982 mA (e) 2920 Ω
- 9.45 $Y = A + \bar{B}$
- 9.47 -0.850 V; 3.59 pJ
- 9.49 359 ns
- 9.50 0 V, -0.600 V, 5.67 mW, 505 Ω , 600 Ω ; $Y = A + B + C$, 5 vs. 6
- 9.53 5.00 k Ω , 5.40 k Ω , 31.6 k Ω , 113 k Ω
- 9.54 1 k Ω , 1 k Ω , 1.30 mW
- 9.56 2.23 k Ω , 4.84 k Ω , 60.1 k Ω
- 9.59 1.446 mA, 1.476 mA, 29.66 μ A; 1.446 mA, 1.476 mA, 29.52 μ A

- 9.61 -0.9 V, -1.1 V, -1.8 V, -2.0 V, -2.7 V, -2.9 V, -4.2 V
- 9.64 $Y = AB + \overline{AC}$
- 9.68 0, -0.8, 0, -0.8, 3.8 V
- 9.69 2.98 pA, 70.5 fA
- 9.71 160; 0.976; 0.976; 0.773 V
- 9.72 0.691 V, 0.710 V
- 9.76 63.3 μA , 265 μA
- 9.78 40.2 mV, 0.617 mV
- 9.80 20.6 mW, 4.22 mW
- 9.82 68.2 mV
- 9.83 2.5 V, 0.15 V, 0.66 V, 0.80 V
- 9.85 44.8 k Ω , 22.4 k Ω
- 9.88 5 V, 0.15 V, 0, -1.06 mA; 31; -1.06 mA vs. -1.01 mA, 0 mA vs. 0.2 mA
- 9.95 8
- 9.97 $R_B \geq 5 \text{ k}\Omega$
- 9.99 7
- 9.100 234 mA, 34.9 mA
- 9.104 (I_B, I_C): (a) (135 μA , -169 μA); (515 μA , 0); (169 μA , 506 μA); (0, 0) (b) all 0 except $I_{B1} = I_{E1} = 203 \mu\text{A}$
- 9.107 180
- 9.108 22
- 9.111 1.85 V, 0.15 V; 62.5 μA , -650 μA ; 13
- 9.113 $Y = \overline{ABC}$; 1.9 V; 0.15 V; 0, -408 μA
- 9.115 1.5 V, 0.25 V; 0, -1.00 mA; 16
- 9.116 0.7 V, 191 μA , 59 μA , 1.18 mA
- 9.117 -1.13 mA, 0, 4.50 mA, 0, 0, 1.80 mA; 0, 0, 0, 0, 1.23 mA, 0
- 9.119 $Y = A + B + C$; 0 V, -0.8 V; -0.40 V
- 9.121 1.05 mA, 26.9 μA
- 9.122 2 fJ; 10 fJ
- 9.124 1.67 ns; 0.5 mW
- 9.126 2.8 ns; 140 mW

Chapter 10

10.2 (a) 41.6 dB, 35.6 dB, 94.0 dB, 100 dB, -0.915 dB

10.4 29.35

10.5 Using MATLAB:

```
t = linspace(0,.004);  
vs = sin(1000*pi*t)+0.333*sin(3000*pi*t)+0.200*sin(5000*pi*t);  
vo = 2*sin(1000*pi*t+pi/6)+sin(3000*pi*t+pi/6)+sin(5000*pi*t+pi/6); plot(t,vs,t,vo)par  
500 Hz: 1 0°, 1500 Hz: 0.333 0°, 2500 Hz: 0.200 0°; 2 30°, 1 30°, 1 30° 2 30°, 3 30°, 5  
30° yes
```

10.7 29.0 dB, 105 dB, 67.0 dB

10.9 19.0 dB, 87.0 dB, 53.0 dB; $V_o = 8.94$ V, recommend ± 10 -V or ± 12 -V supplies

10.11 3.61×10^{-8} S, -7.93×10^{-3} , 1.00, 79.3 Ω

10.13 0.333 mS, -0.333, -1600, 1.78 M Ω

10.15 1.00 mS, -1.00, 3001, 30.0 k Ω

10.16 53.7 dB, 150 dB, 102 dB; 11.7 mV; 31.3 mW

10.17 45.3 mV, 1.00 W

10.21 -5440

10.23 0, ∞ , 80 mW, ∞

10.24 182

10.29 -10 (20 dB), 0.1 V; 0, 0 V

10.31 $v_o = [8 - 4 \sin(1000t)]$ volts; there are only two components; dc: 8 V, 159 Hz: -4 V

10.33 24.1 dB, 2nd and 3rd, 22.4%

10.35 [2.4588](#) 0.0038 [5.3105](#) 0.0066 [1.3341](#) 0.0026 [0.4427](#) 0.0028 [0.0883](#)
0.0012 [0.1863](#) 0.0023

10.37 59.7 dB, 119 dB, 88.9 dB; 5.66 mV

10.41 $R_{id} \geq 4.95$ M Ω

10.43 50 μ V, 140 dB

10.44 (a) -46.8, 4.7 k Ω , 0, 33.4 dB

10.47 (d) $(-1.10 + 0.75 \sin 2500\pi t)$ V

10.49 (a) $v_o = (4.00 - 20V_i \sin 2000\pi t)$ V (b) 0.3 V

10.53 30.1 k Ω , 604 k Ω $A_v = -20.1$, $R_{in} = 30.1$ k Ω

10.56 -70.0, 10 k Ω , 0

- 10.59** 2 M Ω
- 10.60** 83.9, ∞ , 0, 38.5 dB
- 10.63** (d) $(5.28 - 2.88 \sin 3250\pi t)$ V
- 10.67** 2 k Ω , 86.6 k Ω , $A_v = 44.3$
- 10.69** $(-0.47 \sin 3770t - 0.94 \sin 10000t)$ V, 0 V
- 10.70** $-0.3750 \sin 4000\pi t$ V; $-0.6875 \sin 4000\pi t$ V; 0 to -0.9375 V in - 62.5-mV steps
- 10.71** 455/1, 50/1
- 10.72** -10, 110 k Ω , 10 k Ω , $(-30 + 15\cos 8300\pi t)$ V, $(-30 + 30\cos 8300\pi t)$ V
- 10.73** 3.2 V, 3.1 V, 2.82 V, 2.82 V, -1.00 V; 3.82 μ A; 3.80 μ A, 2.80 μ A
- 10.76** 60 dB, 10 kHz, 10 Hz, 9.99 kHz, band-pass amplifier
- 10.77** 80 dB, ∞ , 100 Hz, ∞ , high-pass amplifier
- 10.81** 60 dB, 100 kHz, 28.3 Hz, 100 kHz
- 10.83** Using MATLAB: $n=[1e4 \ 0]$; $d=[1 \ 200*\pi]$; `bode(n,d)`
- 10.86** Using MATLAB: $n=[-20 \ 0 \ -2e13]$; $d=[1 \ 1e4 \ 1e12]$; `bode(n,d)`
- 10.89** $0.030 \sin(2\pi t + 89.4^\circ)$ V, $1.34 \sin(100\pi t + 63.4^\circ)$ V, $3.00 \sin(10^4\pi t + 1.15^\circ)$ V
- 10.92** $0.956 \sin(3.18 \times 10^5\pi t + 101^\circ)$ V, $5.00 \sin(10^5\pi t + 180^\circ)$ V, $5.00 \sin(4 \times 10^5\pi t - 179^\circ)$ V
- 10.94** $A_v(s) = \frac{2 \times 10^8 \pi}{s + 10^7 \pi} \quad | \quad A_v(s) = -\frac{2 \times 10^8 \pi}{s + 10^7 \pi}$
- 10.96** 66 dB, 12.8 kHz, -60 dB/decade
- 10.97** $3.16 \sin(1000\pi t + 10^\circ) + 1.05 \sin(3000\pi t + 30^\circ) + 0.632 \sin(5000\pi t + 50^\circ)$ V
Using MATLAB:
`t = linspace(0,.004);`
`A=10^(10/20);`
`vs = sin(1000*pi*t)+0.333*sin(3000*pi*t)+0.200*sin(5000*pi*t);`
`vo = A*sin(1000*pi*t+pi/18)+3.33*sin(3000*pi*t+3*pi/18)+2.00*sin(5000*pi*t+5*pi/18);`
`plot(t, A*vs, t, vo)`
- 10.98** -4.44 dB, 26.5 kHz
- 10.100** 10 k Ω , 0.015 μ F
- 10.103** 80 dB, 100 Hz
- 10.105** -1.05 dB, 181 Hz
- 10.107** (b) -20.7, 105 kHz
- 10.108** 10.5 k Ω , 105 k Ω , 0.015 μ F

10.113 $T(s) = -sRC$

10.116 $-6.00, 20.0 \text{ k}\Omega, 0; +9.00, 91.0 \text{ k}\Omega, 0; 0, 160 \text{ k}\Omega, 0$

10.117 $1 \text{ A}, 2.83 \text{ V}, > 10 \text{ W}$ (choose 15 W)

10.118 $0.484 \text{ A}; 0.730 \text{ V}; 0.730 \text{ V}; \geq 7.03 \text{ W}$ (choose 10 W), 7.27 W

Chapter 11

- 11.1 (c) 4, 5.00, 4.00, 20 %
- 11.3 120 dB
- 11.4 $1/(1+A\beta)$; 9.99×10^3 percent
- 11.5 (a) 13.49, 9.11×10^{-3} , 0.0675%
- 11.7 120 dB
- 11.9 (a) -9.997, 2.76×10^{-3} , 0.0276%
- 11.13 103 dB
- 11.16 100 μ A, 100 μ A, -48.0 pA, +48.0 pA
- 11.17 (a) 13.5, 296 M Ω , 135 m Ω
- 11.19 (a) -17.4, 2.70 k Ω , 36.8 m Ω
- 11.22 If the gain specification is met with a non-inverting amplifier, the input and output specifications cannot be met.
- 11.24 145V_s, 3.56 Ω
- 11.25 ≤ 0.75 %
- 11.27 (b) shunt-series feedback (d) series-shunt feedback
- 11.29 (a) Series-shunt (a) and series-series (c) feedback
- 11.32 122 dB, 31.5 S
- 11.33 9.96, 6.55 M Ω , 3.19 Ω
- 11.35 9130, 3.00, 3.00, 369 M Ω , 0.398 Ω
- 11.37 (c) $-T/(1+T)$
- 11.39 -9.998 k Ω , 1.200 Ω , 0.1500 Ω
- 11.41 -35.99 k Ω , 4.418 Ω , 0.2799 Ω
- 11.44 -99.91 μ S, 50.04 M Ω , 17.79 M Ω
- 11.49 $10000s/(s + 5000)$, $10000/(2s + 1)$
- 11.54 1.100, 1.899 Ω , 24.65 M Ω
- 11.56 10.96, 35.12 Ω , 3.461 M Ω
- 11.57 680.4, 0.334
- 11.59 330, 0.0260
- 11.61 6.25 %, 16.7 %

- 11.62** 0.00372 %, 0.0183 %
- 11.63** 0 V, -26 mV, 90.9 k Ω
- 11.65** +7500, -0.667 mV
- 11.68** The nearest 5% values are 1 M Ω and 10 k Ω
- 11.70** -6.2 V, 0 V; 10 V, -1.19 V
- 11.72** -5.00 V, 0 V; -10.0 V, 0.182 V
- 11.74** 10 V, 0 V; 15 V, 0.125 V
- 11.77** 110 Ω and 22 k Ω represent the smallest acceptable resistor pair.
- 11.79** 39.2 Ω
- 11.81** 0 V, 3 V; 0.105 V; 0 V; 49.0 dB
- 11.83** (d) $[-0.313 \sin 120\pi t - 4.91 \sin 5000\pi t]$ V
- 11.85** (b) 124 dB
- 11.86** 60 dB
- 11.87** 20.0 k Ω , 56.0 k Ω
- 11.89** 20 Hz
- 11.91** 50 Hz; 5 MHz; 2.5 MHz
- 11.93** 200; 199
- 11.95** 80 dB, 1 kHz, 1 MHz; 101 MHz, 9.90 Hz; 251 MHz, 3.98 Hz
- 11.97** 100 dB, 1 kHz, 1 MHz; 8.4 Hz, 119 MHz; 5.3 Hz, 188 MHz
- 11.99** (a) $R_o(s + \omega_B) / [s + \omega_B(1 + A_o\beta)]$
- 11.102** (a) $R_{id} [s + \omega_B(1 + A_o\beta)] / (s + \omega_B)$
- 11.105** $A_v(s) = -\frac{3.285 \times 10^{12}}{s^2 + 1.284 \times 10^7 s + 1.675 \times 10^{11}}$; (2 poles: 2.08 kHz and 2.04 MHz)
- 11.107** $A_v(s) = -\frac{6.283 \times 10^{10}}{s^2 + 3.142 \times 10^7 s + 6.283 \times 10^5}$; (2 poles: 3.18 mHz and 5.00 MHz)
- 11.109** 6.91, 7.53, 6.35; 145 kHz, 157 kHz, 133 kHz
- 11.111** 2.51 V/ μ s; 2.51 V/ \square s
- 11.113** 10 V/ μ s
- 11.117** 10^{10} Ω , 7.96 pF, 4×10^6 , R_o not specified

- 11.119 90.6°; 90.2°
- 11.120 8.1°; 5.1°
- 11.122 110 kHz; $A \leq 2048$; larger
- 11.123 Yes, but almost no phase margin; 0.4°
- 11.125 75° versus 90°; 65° versus 90°
- 11.128 5 MHz, 90.0°; 2.5 MHz, 90.0°
- 11.130 $A_v(s) = -\frac{5.712 \times 10^6 s}{s^2 + 5.741 \times 10^5 s + 1.763 \times 10^{10}}$; 143°
- 11.132 Yes, but almost no phase margin; 1.83°
- 11.134 90.0°
- 11.136 12°; Yes, 50°
- 11.141 Yes, 24.4°, 50 %
- 11.143 1.8°
- 11.144 38.4°, 31 %
- 11.147 133 pF
- 11.149 90.4°
- 11.152 (a) 72.2°
- 11.153 (a) 11.9 MHz, 5.73°, 85.4%
- 11.155 (a) 70.2, 23.4%
- 11.157 (a) 18.8 MHz

Chapter 12

12.1 A and B taken together, B and C taken together

12.3 -8000 , $2 \text{ k}\Omega$, 0

12.5 48.0 , $968 \text{ M}\Omega$, $46.5 \text{ m}\Omega$

12.7 78.1 dB , $2.00 \text{ k}\Omega$, 0.105Ω

12.8 (c) 2.00 mV , -40.0 mV , $4.00 \mu\text{V}$, 0.800 V , $80.0 \mu\text{V}$, 0 V , -12.0 V , 0.190 V , 0V (ground node)

12.11 -1080 , $3.9 \text{ k}\Omega$, 0

12.12 $8.62 \text{ k}\Omega$, $8.62 \text{ k}\Omega$

12.16 2744 , 2434 , 3094 , $1 \text{ M}\Omega$, $1.02 \text{ M}\Omega$, $980 \text{ k}\Omega$, 0

12.17 -1320 , $75 \text{ k}\Omega$, 0 ; 5.00 mV , 5.00 mV , 55.0 mV , 0 V , -1.10 V , -1.10 V , -6.60 V , 0V (ground node)

12.19 50.0 , 298 kHz ; 48.0 , 349 kHz ; -42.0 , 368 kHz

12.21 14.0 , 286 kHz , 68.8 dB , 146 kHz

12.23 -2380 , $613 \text{ M}\Omega$, $98.0 \text{ m}\Omega$, 29.6 kHz ; 0 V , 10.0 mV , 49.0 mV , $389 \mu\text{V}$, -3.89 V , -3.06 V , -15.0 V , $+15.0 \text{ V}$, -15.0 V , 0 V

12.25 3

12.27 $20 \text{ k}\Omega$, $62 \text{ k}\Omega$, 394 kHz

12.30 103 dB , 98.5 dB , 65 kHz , 38 kHz

12.33 (a) In a simulation of 5000 cases, 33.5% of the amplifiers failed to meet one of the specifications. (b) 1.5% tolerance.

12.36 -12 , $(-6.00 + 1.20 \sin 4000\pi t) \text{ V}$

12.38 4.500 V , 4.99 V , 5.01 V , 5.500 V , 2.7473 V , 2.7473 V , 0.991 V , $-75.4 \mu\text{A}$, $-375 \mu\text{A}$, $+175 \mu\text{A}$, 0.002 , -50.0 , 88 dB

12.40 (b) $0.005 \mu\text{F}$, $0.0025 \mu\text{F}$, $1.13 \text{ k}\Omega$

$$12.44 \quad \frac{V_o}{V_s} = \frac{K}{s^2 R_1 R_2 C_1 C_2 + s [R_1 C_1 (1 - K) + C_2 (R_1 + R_2)] + 1} \quad | \quad S_K^o = \frac{K}{3 - K}$$

12.46 -1

12.48 270 pF , 270 pF , $23.2 \text{ k}\Omega$

12.49 (a) 51.2 kHz , 7.07 , 7.24 kHz

12.52 (a) 1 rad/s, 4.65, 0.215 rad/s; $A_{BP}(s) = \left(\frac{-6s}{s^2 + \frac{s}{3} + 1} \right)^2$

12.54 5.48 kHz, 4.09, 1.34 kHz

12.56 10 k Ω , 100 k Ω , 20 k Ω , 0.0133 μ F

12.58
$$T = +K \frac{\frac{s}{R_2 C_2}}{s^2 + s \left[\frac{1}{R_2 C_2} + \frac{1}{(R_1 \parallel R_2) C_1} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$

12.64 -5.5 V, -5.5, 10 %; -5.0 V, -5.0, 0

12.66 12.6 kHz, 1.58, 7.97 kHz

12.69 (a) -1-125 V (b) -1.688 V

12.70 10.6 mV, 5 %

12.73 455/1, 50/1

12.74 0.31 LSB, 0.16 LSB

12.76 1.43%, 2.5%, 5%, 10%

12.77 11 resistors, 1024:1

12.79 (a) 1.0742 k Ω , 0.188 LSB, 0.094 LSB

12.81 (a) $(2^{n+1}-1)C$

12.84 (b) 2.02 inches

12.85 $3.415469 \text{ V} \leq V_X \leq 3.415781 \text{ V}$

12.86 1.90735 μ V, 11010000101000111101₂, 01111111100111011101₂

12.89 0001011111₂, 95 μ s

12.91 800 kHz, 125 ns

12.93 $v_o(t) = 2.5 \times 10^5 \left(1 - \exp \frac{-t}{5 \times 10^4 RC} \right)$ for $t \geq 0$ | $RC \geq 0.0447 \text{ s}$

12.94 19.1 ns

12.97 1/RC, 2R

12.98 0.5774/RC, 1.83

12.100 60 kHz, 6.8 V

- 12.102** 17.5 kHz, 11.5 V
- 12.106** 0.759 V
- 12.107** 2.4 Hz
- 12.112** $V_O = -V_1V_2/10^4I_S$
- 12.113** 3.11 V, 2.83 V, 0.28 V
- 12.115** 0.445 V, -0.445 V, 0.89 V
- 12.117** 9.86 kHz
- 12.118** $V_O = 0$ is a stable state, so the circuit does not oscillate. $f = 0$.
- 12.120** 0, 0.298 V, 69.0 mV
- 12.122** 13 k Ω , 30 k Ω , 51 k Ω , 150 pF

Chapter 13

- 13.1** $(0.700 + 0.005 \sin 2000\pi t)$ V, $-1.03 \sin 2000\pi t$ V, $(5.00 - 1.03 \sin 2000\pi t)$ V. 2.82 mA
- 13.3** (a) C_1 is a coupling capacitor that couples the ac component of v_1 into the amplifier. C_2 is a coupling capacitor that couples the ac component of the signal at the collector to the output v_O . C_3 is a bypass capacitor. (b) The signal voltage at the top of resistor R_4 will be zero.
- 13.5** (a) C_1 is a coupling capacitor that couples the ac component of v_1 into the amplifier. C_2 is a bypass capacitor. C_3 is a coupling capacitor that couples the ac component of the signal at the drain to output v_O . (b) The signal voltage at the source of M_1 will be $v_s = 0$.
- 13.7** (a) C_1 is a coupling capacitor that couples the ac component of v_1 into the amplifier. C_2 is a bypass capacitor. C_3 is a coupling capacitor that couples the ac component of the signal at the collector to output v_O . (b) The signal voltage at the emitter terminal will be $v_e = 0$.
- 13.9** (a) C_1 is a coupling capacitor that couples the ac component of v_1 into the amplifier. C_2 is a coupling capacitor that couples the ac component of the signal at the drain to output v_O .
- 13.13** (a) C_1 is a coupling capacitor that couples the ac component of v_1 into the amplifier. C_2 is a bypass capacitor. C_3 is a coupling capacitor that couples the ac component of the signal at the drain to the output v_O . (b) The signal voltage at the top of R_4 will be zero.
- 13.16** (1.46 mA, 5.36 V)
- 13.18** (19.2 μ A, 6.37 V)
- 13.20** (62.2 μ A, 43.65 V)
- 13.24** (91.3 μ A, 6.05 V)
- 13.28** (245 μ A, 3.73 V)
- 13.32** (423 μ A, -6.76 V)
- 13.34** (1.25 mA, 8.63 V)
- 13.46** Thévenin equivalent source resistance, gate-bias voltage divider, gate-bias voltage divider, source-bias resistor—sets source current, drain-bias resistor—sets drain-source voltage, load resistor
- 13.51** 118 Ω , 3.13 T Ω , ≤ -28.5 mV
- 13.52** (c) 8.65 Ω
- 13.53** Errors: +10.7%, -9.37%; +23.0%, - 17.5%

- 13.54** (c) 1.25 μA
- 13.55** (213 μA , $\geq 0.7\text{ V}$), 8.52 mS, 469 $\text{k}\Omega$
- 13.60** (b) +16.7%, -13.6%
- 13.61** 90, 120; 95, 75
- 13.66** [-76.7, -75.8]
- 13.68** -40.0
- 13.72** -90
- 13.74** Yes, using $I_C R_C = (V_{CC} + V_{EE})/2$
- 13.76** 3
- 13.77** 20 mA; 24.7 V
- 13.78** 0.500 V
- 13.79** No, there will be significant distortion
- 13.80** -263
- 13.85** 32/1, 0.500 V
- 13.86** 0.800 A
- 13.87** 10%, 20%
- 13.90** (78 μA , 9 V)
- 13.91** Virtually any desired Q-point
- 13.92** $400 = 133,000i_P + v_{PK}$; (1.4 mA, 215 V); 1.6 mS, 55.6 $\text{k}\Omega$, 89.0; -62.7
- 13.93** FET
- 13.94** BJT
- 13.95** 37.5 μA , 2400
- 13.96** 2000, 200, 8.00 mS, 0.800 mS
- 13.99** 23.5 dB
- 13.101** (142 μA , 7.5 V)
- 13.102** 0.300 V
- 13.103** 1.0 V, 56 V
- 13.105** 3
- 13.107** -11.0
- 13.110** -7.28

- 13.115 29.4 k Ω , 93.4 k Ω
- 13.118 833 k Ω , 1.46 M Ω
- 13.120 243 k Ω , 40.1 k Ω
- 13.122 6.8 M Ω , 45.8 k Ω , independent of K_n
- 13.124 1 M Ω , 3.53 k Ω
- 13.125 $-281v_i$, 3.74 k Ω
- 13.127 $-23.6v_i$, 508 k Ω
- 13.129 38.9 dB, 6.29 k Ω , 9.57 Ω
- 13.131 36.4 dB, 62.9 k Ω , 95.7 k Ω
- 13.135 138 μ W, 182 μ W, 1.28 mW, 0.780 mW, 0.820 mW, 3.19 mW
- 13.139 0.552 mW, 0.684 mW, 0.225 mW, 18.7 μ W, 50.4 μ W, 1.53 mW
- 13.142 $V_{CC}/15$
- 13.143 3.38 V, 13.6 V
- 13.144 $(V_{CC})^2/8R_L$, $(V_{CC})^2/2R_L$, 25%
- 13.145 0.992 V
- 13.147 2.24 V
- 13.148 1.65 V
- 13.149 2.93 V
- 13.153 833 μ A
- 13.154 -4.60, 1 M Ω , 6.82 k Ω

Chapter 14

- 14.1 (a) C-C or emitter-follower (c) C-E (e) not useful, signal is being injected into the drain (h) C-B (k) C-G (o) C-D or source-follower
- 14.14 -32.6 , $9.58 \text{ k}\Omega$, $596 \text{ k}\Omega$, -27.1 ; -17.2 , $11.6 \text{ k}\Omega$, $1060 \text{ k}\Omega$, -17.1
- 14.15 -3.77 , $2 \text{ M}\Omega$, $26.5 \text{ k}\Omega$, -3770 ; -8.03 , $2 \text{ M}\Omega$, $10.0 \text{ k}\Omega$, -10000
- 14.16 (a) -6.91 (e) -240
- 14.17 $3.3 \text{ k}\Omega$, $33 \text{ k}\Omega$
- 14.20 -178 , 58 , $21.4 \text{ k}\Omega$, $39 \text{ k}\Omega$, 5.13 mV
- 14.21 121 , 62 , $2.84 \text{ k}\Omega$, $7.58 \text{ k}\Omega$, 6.76 mV , -120
- 14.22 -12.3 , -9.62 , $368 \text{ k}\Omega$, $82 \text{ k}\Omega$, 141 mV , -7.50
- 14.24 -2.74 , -762 , $10 \text{ M}\Omega$, $1.80 \text{ k}\Omega$, 0.800 V
- 14.25 -3790 , -5.44 , $1.30 \text{ k}\Omega$, $68.5 \text{ k}\Omega$, 5.96 mV
- 14.27 0.747 , $29.8 \text{ k}\Omega$, $104 \text{ }\Omega$, 29.7
- 14.28 0.896 , $2 \text{ M}\Omega$, $125 \text{ }\Omega$, $16,000$
- 14.29 0.987 , $44.8 \text{ k}\Omega$, $15.2 \text{ }\Omega$, 1.54 V
- 14.30 0.960 , $1 \text{ M}\Omega$, $507 \text{ }\Omega$, 6.19 V
- 14.31 0.992 , $12.6 \text{ M}\Omega$, $1.32 \text{ k}\Omega$, 0.601 V
- 14.32 ∞ , $7.94 \text{ M}\Omega$, $247 \text{ }\Omega$, ∞
- 14.33 $v_i \leq (0.005 + 0.2V_{R_E}) \text{ V}$
- 14.35 0.9992 , 30.1 V
- 14.37 190 , $980 \text{ }\Omega$, $2.52 \text{ M}\Omega$, 0.990 ; 62.1 , $980 \text{ }\Omega$, $7.57 \text{ M}\Omega$, 0.969
- 14.38 39.4 , $1.20 \text{ k}\Omega$, ∞ , 0.600 ; 7.94 , $1.43 \text{ k}\Omega$, ∞ , 0.714
- 14.41 40.7 , $185 \text{ }\Omega$, $39.0 \text{ k}\Omega$, 18.5 mV
- 14.42 4.11 , $1.32 \text{ k}\Omega$, $20 \text{ k}\Omega$, 354 mV
- 14.43 5.01 , $3.02 \text{ k}\Omega$, $24 \text{ k}\Omega$, 352 mV
- 14.46 $32.1 \text{ }\Omega$, $260 \text{ }\Omega$
- 14.47 $633 \text{ }\Omega$, $353 \text{ }\Omega$
- 14.49 $(\beta_o + 1)r_o = 244 \text{ M}\Omega$

14.51 Low R_{in} , high gain: Either a common-base amplifier operating at a current of 71.4 μA or a common-emitter amplifier operating at a current of approximately 7.14 mA can meet the specifications with $V_{CC} \approx 14 \text{ V}$.

14.53 Large R_{in} , moderate gain: Common-source amplifier.

14.55 Common-drain amplifier.

14.56 Low R_{in} , high gain: Common-emitter amplifier with 5- Ω input "swamping" resistor.

14.57 Cannot be achieved with what we know at this stage in the text.

14.59 1.66 Ω

14.62

v_i	1 kHz	2 kHz	3 kHz	THD
5 mV	621 mV	26.4 mV (4.2%)	0.71 mV (0.11%)	4.2%
10 mV	1.23 V	0.104 V (8.5%)	5.5 mV (0.45%)	8.5%
15 mV	1.81 V	0.228 V (12.6%)	18.2 mV (1.0%)	12.7%

14.64 (b) $479v_i$, 384 k Ω

14.65 v_i , 297 Ω

14.68 g_m , 0; 400 μS , 0

14.70 $-g_m \left(1 + \frac{1}{\mu_f}\right) \mid -g_o \mid \mu_f + 1 ; -502 \mu\text{S}, -2.00 \mu\text{S}$

14.71 $-\frac{g_m}{1 + g_m R_E} \mid -\frac{g_o}{(1 + g_m R_E)} \left(\frac{R_E}{R_E + r_\pi}\right) \mid \frac{G_m}{G_r} = \mu_f \left(1 + \frac{r_\pi}{R_E}\right) \gg 1$

14.74 -0.984, 0.993, 0.766 V

14.76 SPICE: (116 μA , 7.53 V), -150, 19.6 k Ω , 37.0 k Ω

14.78 SPICE: (115 μA , 6.30 V), -20.5, 368 k Ω , 65.1 k Ω

14.80 SPICE: (66.7 μA , 4.47 V), -16.8, 1.10 M Ω , 81.0 k Ω

14.83 SPICE: (5.59 mA, -5.93 V), -3.27, 10.0 M Ω , 1.52 k Ω

14.85 SPICE: (6.20 mA, 12.0 V), 0.953, 2.00 M Ω , 388 Ω

14.86 SPICE: (175 μA , 4.29 V), -4.49, 500 k Ω , 17.0 k Ω

14.87 (430 μA , 1.97 V), (430 μA , 3.03 V), -2.89, 257 k Ω , 3.22 k Ω , (Note $A_{tr} = 743 \text{ k}\Omega$)

14.88 (4.50 mA, 2.50 V), (4.50 mA, 2.50 V), -83.5, 6.63 k Ω , 10.3 k Ω ,

14.89 0.485, 182 k Ω , 435 Ω

14.92 1.80 μF , 0.068 μF , 120 μF ; 2.7 μF

- 14.94** 0.20 μF , 270 $\square\text{F}$; 100 μF , 0.15 μF
- 14.96** 1.5 μF , 0.027 μF
- 14.98** 8200 pF, 820 pF
- 14.102** 33.3 mA
- 14.103** $R_1 = 120 \text{ k}\Omega$, $R_2 = 110 \text{ k}\Omega$
- 14.106** $45.1 \leq A_v \leq 55.3$ - Only slightly beyond the limits in the Monte Carlo results.
- 14.108** The second MOSFET
- 14.111** The supply voltage is not sufficient - transistor will be saturated.
- 14.113** 4.08, 1.00 $\text{M}\Omega$, 64.3 Ω
- 14.116** 2.17, 1.00 $\text{M}\Omega$, 64.3 Ω
- 14.121** 468, 73.6 $\text{k}\Omega$, 18.8 $\text{k}\Omega$
- 14.122** 0.670, 107 $\text{k}\Omega$, 20.0 $\text{k}\Omega$
- 14.124** 7920, 10.0 $\text{k}\Omega$, 18.8 $\text{k}\Omega$
- 14.125** 140, 94.7 Ω , 113 Ω
- 14.127** 19.2 Hz; 18.0 Hz
- 14.129** 1.56 Hz; 1.22 Hz
- 14.131** 6.40 Hz; 5.72 Hz
- 14.133** 0.497 Hz, 0.427 Hz
- 14.134** 1.70 kHz; 1.68 kHz

Chapter 15

- 15.1** (26.2 μA , 7.08 V); -346, 191 k Ω , 660 k Ω ; -0.604, 49.2 dB, 27.3 M Ω
- 15.2** (5.25 μA , 1.68 V); -21.0, -0.636, 24.4 dB, 572 k Ω , 4.72 M Ω , 200 k Ω , 50.0 k Ω
- 15.4** (85.6 μA , 10.1 V); -342, -0.494, 50.8 dB, 58.4 k Ω , 10.1 M Ω , 200 k Ω , 50.0 k Ω
- 15.7** $R_{EE} = 1.1 \text{ M}\Omega$, $R_C = 1.0 \text{ M}\Omega$
- 15.8** (a) (198 μA , 3.39 V); differential output: -372, 0, ∞ (b) single-ended output: -186, -0.0862, 66.7 dB; 25.2 k Ω , 27.3 M Ω , 94.0 k Ω , 13.5 k Ω
- 15.9** 2.478 V, 6.258 V, -2.78 V, 4.64 V
- 15.11** $V_O = 5.99 \text{ V}$, $v_o = 0$; $V_O = 5.99 \text{ V}$; $v_o = 1.80 \text{ V}$; 33.3 mV
- 15.15** (37.4 μA , 5.22 V); Differential output: -300, 0, ∞ ; single-ended output: -150, -0.661, 47.2 dB; 200 k Ω , 22.7 M Ω
- 15.16** -5.850 V, -3.450 V, -2.40 V
- 15.18** (4.94 μA , 1.77 V); differential output: -77.2, 0, ∞ ; single-ended output: -38.6, -0.0385, 60.0 dB; 810 k Ω , 405 M Ω , [-1.07 V, 1.60 V]
- 15.21** -283, -.00494, 95.2 dB
- 15.22** -273.6, -.004429, 94.9 dB
- 15.24** (107 μA , 10.1 V); differential output: -18.2, 0, ∞ ; single-ended output: -9.10, -0.487, 25.4 dB; ∞ , ∞
- 15.27** 2.4 k Ω , 5.6 k Ω
- 15.31** (150 μA , 5.62 V); differential output: -26.0, 0, ∞ ; single-ended output: -13.0, -0.232, 35.0 dB; ∞ , ∞
- 15.34** (20.0 μA , 9.05 V); differential output: -38.0, 0, ∞ ; single-ended output: -19.0, -0.120, 44.0 dB; ∞ , ∞
- 15.35** 312 μA , 27 k Ω
- 15.38** -20.26, -0.7812, 22.3 dB, ∞ , ∞
- 15.40** -3.80 V, -2.64 V, 48.3 mV
- 15.44** -79.9, -0.494, 751 k Ω
- 15.45** (99.0 μA , 8.80 V), -30.4, -0.167, 550 k Ω
- 15.47** (49.5 μA , 3.29 V), (49.5 μA , 8.70 V); -149, -0.0625, 101 k Ω
- 15.48** (100 μA , 1.20 V), (100 μA , 3.18 V); -13.4, 0, ∞
- 15.51** (24.8 μA , 15.0 V), (625 μA , 15.0 V); 896, 202 k Ω ; 20.0 k Ω ; 153 M Ω ; v_2
- 15.52** [-13.6 V, 14.3 V]

- 15.57** (24.8 μA , 14.3 V), (4.95 μA , 14.3 V), (495 μA , 15.0 V); 5010, 202 k Ω ; 19.4 k Ω ; 150 M Ω ; v_2
- 15.58** (98.8 μA , 17.1 V), (360 μA , 17.1 V); 620, 40.5 k Ω ; 48.8 k Ω ; 37.5 M Ω ; v_2
- 15.59** [-16.6 V, 16.4 V]
- 15.63** (98.8 μA , 15.3 V), (300 μA , 15.3 V); 27700, 40.5 k Ω ; 2.59 M Ω
- 15.67** (250 μA , 18.6 V), (500 μA , 18.0 V); 4490, ∞ ; 170 k Ω
- 15.69** 5770
- 15.71** (250 μA , 7.42 V), (6.10 μA , 4.30 V), (494 μA , 5.00 V); 4230, ∞ ; 97.5 k Ω
- 15.75** (49.5 μA , 18.0 V), (360 μA , 17.3 V), (990 μA , 18.0 V); 12700, 101 k Ω ; 1.88 k Ω ; 69.2 M Ω ; v_2
- 15.77** (300 μA , 5.10 V), (500 μA , 2.89 V), (2.00 mA, 5.00 V); 528, ∞ , 341 Ω
- 15.79** (300 μA , 5.55 V), (500 μA , 2.89 V), (2.00 mA, 5.00 V), 2930, ∞ , 341 Ω
- 15.81** (250 μA , 10.9 V), (2.00 mA, 9.84 V), (5.00 mA, 12.0 V); 868, ∞ ; 127 Ω
- 15.82** (99.0 μA , 4.96 V), (99.0 μA , 5.00 V), (500 μA , 3.41V), (2.00 mA, 5.00 V); 11400, 50.5 k Ω , 224 Ω
- 15.84** (49.5 μA , 11.0 V), (98.0 μA , 10.3 V), (735 μA , 16.0 V); 2680, 101 k Ω , 3.05 k Ω ; $\square\square\square\square\square\square\square\square\square$ d for an ideal current source, 10.3 V]; 1.44 mV
- 15.86** No, R_{id} must be reduced or R_{out} must be increased.
- 15.88** (24.8 μA , 17.3 V), (24.8 μA , 17.3 V), (9.62 μA , 15.9 V), (490 μA , 16.6 V), (49.0 μA , 17.3 V), (4.95 mA, 18.0 V); 88.5 dB, 202 k Ω , 22.0 Ω
- 15.90** 250 $\mu\text{A}/\text{V}^2$; 280; 868
- 15.92** 196; 896
- 15.94** 0.9996, 239 M Ω , 21.2 Ω
- 15.96** 9.992, 67.6 M Ω , 1.48 Ω
- 15.98** 36.8 μA
- 15.101** 391 μA
- 15.104** 22.8 μA
- 15.106** 5 mA, 0 mA, 10 mA, 12.5 percent
- 15.107** 66.7 percent
- 15.110** 46.7 mA, 13.5 V
- 15.112** 23.5 μA

- 15.113 6.98 mA, 0 mA
- 15.114 25.0 m Ω
- 15.116 (a) 18.7 μ A, 61.5 M Ω
- 15.118 (a) 134 μ A, 8.19 M Ω
- 15.120 Two of many: 75 k Ω , 6.2 k Ω , 150 Ω ; 68 k Ω , 12 k Ω , 1 k Ω
- 15.122 59.4 μ A, 15.7 M Ω
- 15.123 0, ∞
- 15.125 88.6 μ A, 18.6 M Ω
- 15.127 17.0 μ A, 131 M Ω
- 15.130 390 k Ω , 210 k Ω , 33 k Ω
- 15.132 157.4 μ A, 16.61 M Ω , 31.89 μ A, 112.2 M Ω
- 15.133 44.1 μ A, 22.1 M Ω , 10.1 μ A, 209 M Ω
- 15.136 400 μ A, 2.89×10^{11} Ω
- 15.137 (4.64 μ A, 7.13 V), (9.38 μ A, 9.02 V); 40.9 dB, 96.5 dB
- 15.140 $\beta_{o1}\mu_{f1}/2$, For typical numbers: 20(100)(70) = 140,000 or 103 dB
- 15.141 3σ limits: $I_o = 199 \mu\text{A} \pm 32.5 \mu\text{A}$, $R_{\text{OUT}} = 11.8 \text{ M}\Omega \pm 2.6 \text{ M}\Omega$
 3σ limits: $I_o = 201 \mu\text{A} \pm 34.7 \mu\text{A}$, $R_{\text{OUT}} = 21.7 \text{ M}\Omega \pm 3.6 \text{ M}\Omega$

Chapter 16

- 16.1 [4.28 k Ω , 4.50 k Ω]
16.2 2.50 mV; 5.02 mV; 1%
16.4 7.7%, 0.813 μ A, 0.855 μ A, ($I_{OS} = -42.0$ nA)
16.7 25.0 mV; 1.2%; 0.4%
16.8 (a) 94.8 μ A, 186 μ A, 386 μ A, 1.16 M Ω , 580 k Ω , 290 k Ω
16.11 87.5 μ A, 175 μ A, 350 μ A; 0.0834 LSB, 0.126 LSB, 0.411 LSB
16.12 316 μ A, 332 k Ω , 662 μ A, 166 k Ω
16.16 (a) 693 μ A, 93.8 k Ω , 1.11 mA, 56.8 k Ω
16.18 422 k Ω , 112 μ A; 498 k Ω , 112 μ A
16.21 202 μ A, 327 μ A
16.22 472 μ A, 759 μ A; 479 μ A, 759 μ A; 430 μ A, 692 μ A
16.24 63.8 k Ω , 11.8 μ A, 123 μ A
16.26 10
16.28 15 k Ω , 2/3
16.30 138 μ A, 514 M Ω
16.32 4.90 k Ω
16.34 172 k Ω , 15.0 k Ω , 0.445
16.36 21.8 μ A, 18.4 M Ω ; 43.7 μ A, 9.17 M Ω
16.38 29.8 μ A, 92.9 M Ω ; 87.9 μ A, 31.5 M Ω ; 2770; 1.40 V
16.42 17.0 μ A, 80/1; 89.9 M Ω
16.44 $2/g_{m2}$
16.46 5.49/1
16.49 11.7 M Ω , 0, 6.687, 90.4 M Ω
16.51 1.33 M Ω , 1, 126, 84.4 M Ω
16.52 20.0 μ A, 953 M Ω ; 19.1 kV; 2.21 V
16.54 21.0 μ A, 4.40 nA
16.57 (b) 50 μ A, 240 M Ω ; 12.0 kV; 3.05 V
16.60 16.9 μ A, 163 M Ω , 2750 V; $2V_{BE} = 1.40$ V
16.62 2.86 k Ω

- 16.64** (a) $102 \text{ G}\Omega$
- 16.66** (a) $51.0 \text{ G}\Omega$
- 16.68** (a) $64.0 \text{ }\mu\text{A}$, $3.10 \text{ M}\Omega$
- 16.70** $5.71 \text{ k}\Omega$
- 16.72** $317 \text{ }\mu\text{A}$; $295 \text{ }\mu\text{A}$; $66.5 \text{ }\mu\text{A}$
- 16.74** $\cong \beta_{\delta} r_{o4} / 2$
- 16.76** $14.5 \text{ k}\Omega$, $226 \text{ k}\Omega$
- 16.78** $11.5 \text{ k}\Omega$, $313 \text{ k}\Omega$
- 16.80** $I_{C1} = 137 \text{ }\mu\text{A}$, $I_{C1} = 44.8 \text{ }\mu\text{A}$, $S_{V_{CC}}^{I_{C1}} = 4.40 \times 10^{-2}$, $S_{V_{CC}}^{I_{C2}} = 1.54 \times 10^{-2}$
- 16.82** $n > 1/3$
- 16.84** 6.24 mA
- 16.86** (b) $I_{D1} = 8.19 \text{ }\mu\text{A}$ $I_{D2} = 7.24 \text{ }\mu\text{A}$ $S_{V_{DD}}^{I_{D1}} = 7.75 \times 10^{-2}$ $S_{V_{DD}}^{I_{D2}} = 6.31 \times 10^{-2}$
 The currents differ considerably from the hand calculations. The currents are quite sensitive to the value of λ . The hand calculations used $\lambda = 0$. If the simulations are run with $\lambda = 0$, then the results are identical to the hand calculations.
- 16.88** $14.4 \text{ }\mu\text{A}$, $36.0 \text{ }\mu\text{A}$, $6.56 \text{ }\mu\text{A}$, $72.0 \text{ }\mu\text{A}$, $9.48 \text{ }\mu\text{A}$
- 16.90** $I_{C2} = 16.9 \text{ }\mu\text{A}$ $I_{C1} = 31.5 \text{ }\mu\text{A}$ - Similar to hand calculations.
 $S_{V_{CC}}^{I_{C1}} = 9.36 \times 10^{-3}$ $S_{V_{CC}}^{I_{C2}} = 2.64 \times 10^{-3}$
- 16.92** (a) $388 \text{ }\mu\text{A}$, $259 \text{ }\mu\text{A}$
- 16.94** $110 \text{ }\mu\text{A}$
- 16.96** 4.90 V , 327.4 K
- 16.98** 1.20 V , 304.9 K
- 16.100** 5.07 V , $+44.0 \text{ }\mu\text{V/K}$
- 16.102** $-472 \text{ }\mu\text{V/K}$, $-199 \text{ }\mu\text{V/K}$
- 16.104** $2.248 \text{ k}\Omega$, $10.28 \text{ k}\Omega$, $80 \text{ k}\Omega$, $23.9 \text{ k}\Omega$, $126 \text{ k}\Omega$
- 16.105** 79.1 , 6.28×10^{-5} , 122 dB
- 16.107** 47.2 , 6.97×10^{-5} , 117 dB
- 16.109** 1200 , 4×10^{-3} , 110 dB , $\pm 2.9 \text{ V}$
- 16.113** $(100 \text{ }\mu\text{A}, 8.70 \text{ V})$, $(100 \text{ }\mu\text{A}, 7.45 \text{ V})$, $(100 \text{ }\mu\text{A}, -2.50 \text{ V})$, $(100 \text{ }\mu\text{A}, -1.25 \text{ V})$, 324 , 152
- 16.115** $(125 \text{ }\mu\text{A}, 1.54 \text{ V})$, $(125 \text{ }\mu\text{A}, -2.79 \text{ V})$, $(125 \text{ }\mu\text{A}, 2.50 \text{ V})$, $(125 \text{ }\mu\text{A}, 1.25 \text{ V})$; 19600

- 16.118 171 μA
- 16.119 (b) 100 μA
- 16.120 (250 μA , 5.00 V), (250 μA , 5.00 V), (250 μA , -1.75 V), (250 μA , -1.75 V), (500 μA , -3.21 V), (135 μA , 5.00 V), (135 μA , -5.00 V), (250 μA , 2.16 V), (500 μA , 3.25 V), (500 μA , 3.21 V), (500 μA , 3.58 V); 4130; 2065
- 16.122 12,600
- 16.124 (250 μA , 7.50 V), (250 μA , 7.50 V), (250 μA , -1.75 V), (250 μA , -1.75 V), (1000 μA , -5.13 V), (330 μA , 7.50 V), (330 μA , -7.50 V), (1000 μA , 4.75 V), (250 μA , 2.16 V), (500 μA , 5.75 V), (1000 μA , 5.13 V), 3160
- 16.126 (b) 42.9/1 (c) 23000
- 16.130 7.78, 574 Ω , 3.03×10^5 , 60.0 k Ω
- 16.132 ± 1.4 V, ± 2.4 V
- 16.133 (a) 9.72 μA , 138 μA , 46.0 μA
- 16.134 271 k Ω , 255 Ω
- 16.136 $V_{EE} \geq 2.8$ V, $V_{CC} \geq 1.4$ V; 3.8 V, 2.4 V
- 16.138 2.84 M Ω , 356 k Ω . 6.11×10^5
- 16.141 100 μA , 15.7 V), (100 μA , 15.7 V), (50 μA , -12.9 V), (50 μA , -0.700 V), (50 μA , -0.700 V), (50 μA , -12.9 V), (50 μA , 1.40 V), (50 μA , 1.40 V), (2.00 μA , 29.3 V), (100 μA , 0.700 V), (100 μA , 13.6 V); 1.00 mS, 752 k Ω
- 16.142 (50 μA , 15.7 V), (50 μA , 15.7 V), (50 μA , 12.9 V), (50 μA , 12.9 V), (50 μA , 1.40 V), (50 μA , 1.40 V), (1.00 μA , 29.3 V), (100 μA , 1.40 V), (1 μA , 0.700 V), (1 μA , 13.6 V); 1.00 mS, 864 k Ω
- 16.143 (50 μA , 2.50 V), (25 μA , 3.20 V)
- 16.144 (a) 125 μA , 75 μA , 62.5 μA , 37.5 μA ,
- 16.146 $(500 - 195 \sin 5000\pi t) \mu\text{A}$, $(500 + 195 \sin 5000\pi t) \mu\text{A}$; 0.488 mS

Chapter 17

17.1 $A_{mid} = 50$, $F_L(s) = \frac{s^2}{(s+4)(s+30)}$, yes, $A_v(s) \approx 50 \frac{s}{(s+30)}$, 4.77 Hz, 4.82 Hz

17.4 200, $\frac{1}{\left(\frac{s}{10^4} + 1\right)\left(\frac{s}{10^5} + 1\right)}$, yes, 1.59 kHz, 1.58 kHz

17.7 200, $\frac{s^2}{(s+1)(s+2)}$, $\frac{1}{\left(1 + \frac{s}{500}\right)\left(1 + \frac{s}{1000}\right)}$, 0.356 Hz, 142 Hz; 0.380 Hz, 133 Hz

17.9 (b) -14.3 (23.1 dB), 11.3 Hz

17.10 (b) -15.6, 8.15 Hz

17.11 1.52 μF ; 1.50 μF , 49.4 Hz

17.13 0.213 μF ; 0.22 μF ; 1940 Hz

17.14

$$A_v(s) = A_{mid} \frac{s^2}{(s + \omega_1)(s + \omega_2)} \quad \left| \quad \omega_1 = \frac{1}{C_1 \left(R_S + R_E \parallel \frac{1}{g_m} \right)} \quad \left| \quad \omega_2 = \frac{1}{C_2 (R_C + R_3)} \quad \left| \quad 2 \text{ zeros at } \omega = 0 \right. \right.$$

35.5 dB, 13.2 Hz; -5.0 V, 7.9 V

17.16 123 Hz; 91 Hz; (145 μA , 3.57 V)

17.18 -131, 49.9 Hz, 12.0 V

17.19 45.5 Hz

17.21 7.23 dB, 19.8 Hz

17.23 0.739, 11.9 Hz, 10.0 V

17.24 0.15 μF

17.25 1.8 μF

17.27 Cannot reach 2 Hz; $f_L = 13.1$ Hz for $C_1 = \infty$, limited by C_3

17.29 0.15 μF

17.30 308 ps

17.33 (a) 22.5 GHz

17.34 -96.7; -110

17.35 0.978; 0.979

- 17.37 (a) -5100, -98.0, -5000, -100, 2% error (b) -350, -42.9, -300, -50, 18% error
- 17.39 Real roots: -100, -20, -15, -5
- 17.41 (3.31 mA, 2.71 V); -89.6, 1.45 MHz; 130 MHz
- 17.43 -14.3, 540 kHz
- 17.45 (0.834 mA, 2.41 V); -8.27, 3.29 MHz; 27.2 MHz
- 17.49 61.0 pF, 303 MHz
- 17.52 $1/10^5 RC$; $1/10^6 RC$; $-1/sRC$
- 17.54 39.2 dB, 5.51 MHz
- 17.56 -114, 1.11 MHz; 127 MHz, 531 MHz
- 17.59 680Ω , -18.0, 92.7 MHz
- 17.60 -29.3, 7.41 MHz, 227 MHz
- 17.62 300Ω , $1 \text{ k}\Omega$
- 17.63 -1300; -92.3; -100, -1200
- 17.64 9.55, 64.4 MHz
- 17.66 59.7, 1.72 MHz
- 17.69 2.30, 14.1 MHz
- 17.70 3.17, 14.1 MHz, 15.4 Hz
- 17.71 0.960, 114 MHz
- 17.74 -1.56 dB, 73.3 MHz
- 17.75 $C_{GD} + C_{GS}/(1 + g_m R_L)$ for $\omega \ll \omega_T$
- 17.77 Using a factor of 2 margin: 8 GHz, 19.9 ps
- 17.81 672 mA - not a realistic design. A different FET is needed.
- 17.83 393 kHz; 640 kHz
- 17.87 294 kHz
- 17.89 48.2 kHz
- 17.90 52.9 kHz
- 17.92 (a) 568 kHz
- 17.94 (a) 2.01 MHz
- 17.96 53.4 dB, 833 Hz, 526 kHz
- 17.97 1.52 MHz; $323 \mu\text{H}$, 3.65 MHz
- 17.99 -45° ; -118° ; -105°

- 17.101 22.5 MHz, -41.1, 2.91
- 17.102 20.1 pF; 12.6; $n = 2.81$; 21.8 pF
- 17.103 15.2 MHz; 27.5 MHz
- 17.104 13.4 MHz, 7.98, $112/\underline{-90^\circ}$; 4.74 MHz, 5.21, $46.1/\underline{-90^\circ}$
- 17.105 10.1 MHz, 3.96, -35.3; 10.94 MHz, 16.8, -75.1
- 17.108 65 pF; 240, -4.41×10^4 , 25.1 kHz
- 17.110 62.3 pF; 152 kHz, 40
- 17.112 (b) 497 Ω , 108 pF
- 17.113 100 Ω , 104 fF; 52.2 Ω , 144 fF
- 17.117 (a) 100 MHz, 1900 MHz
- 17.119 58.9 dB
- 17.121 -19.5 dB; -23.9 dB
- 17.123 0.6 A
- 17.125 -13.5 dB; -17.9 dB
- 17.127 0.2 A
- 17.129 1, 0.5, 0.5
- 17.131 0.567 V
- 17.133 $0.2I_1R_C$

Chapter 18

18.1 (b) 200, 4.975, 0.498%

18.3 1/40, 790.6, -38.95

18.5 104 dB

18.7 $1/(1+T)$; 0.0498 %

18.9 (a) Series-shunt feedback (b) Shunt-series feedback

18.13 857 Ω , 33.3, 57.1, 506 Ω

18.15 245 Ω , 0, 0.952, 126 Ω

18.17 8.33×10^5 , 16.7 S

18.19 12.9, 8.88 M Ω , 1.52 Ω

18.21 31.1 Ω , 2.01, 17.9, 195 Ω

18.23 10.1, 252 k Ω , 358 Ω

18.25 2.66 Ω ; (32.2 Ω , 0, 11.1)

18.27 141 Ω ; (13.0 k Ω , 0, 91.2)

18.29 0.9987, 110.4 M Ω , 2.845 Ω vs. 0.999, 108 M Ω , 2.70 Ω

18.31 -39.0 k Ω , 8.31 Ω , 0.295 Ω

18.33 33.2 Ω , 45.6 Ω , -38.9 k Ω

18.35 29.7 k Ω , 1.48 k Ω , -672 k Ω

18.37 0.133 mS, 60.4 M Ω , 26.8 M Ω

18.39

SPICE Results: $A_{tc} = 9.92 \times 10^{-5}$ S $R_{in} = 144.1$ M Ω $R_{out} = 11.91$ M Ω

Hand Calculations: $A_{tc} = 9.92 \times 10^{-5}$ S $R_{in} = 148$ M Ω $R_{out} = 11.1$ M Ω

18.41 0.467 mS, 95.0 M Ω

18.42 8.48, 15.1 Ω , 3.51 M Ω

18.43 400 Ω , 12.5 M Ω , 0.992

18.45 29.8 M Ω , 799 M Ω , 1.08 G Ω

18.47 2.97, 14.5 Ω , 24.3 M Ω ; 2.99, 14.6 Ω , 18.1 M Ω

18.49 30.39 G Ω ; 33.3 G Ω

18.51 47.32 M Ω ; 37.5 M Ω

18.53 $T_v = 105$, $T_i = 18.1$, $T = 15.2$, $R_2/R_1 = 5.55$

- 18.55** $T_v = 988$, $T_i = 109$, $T = 98.0$, $R_2/R_1 = 8.99$
- 18.57** 110 kHz, 2048, ≤ 2048
- 18.59** 219 pF
- 18.61** 76.6°
- 18.63** 107°
- 18.67** 9.38 MHz, 41.7 V/ μ S
- 18.69** (b) 95.5 MHz, 30 V/ μ S
- 18.71** ± 8.57 V/ μ S
- 18.73** 71.5 MHz, 11.4 kHz, 236 MHz, 326 MHz, 300 MHz; 84.4 dB; < 0 ; 16.8 pF
- 18.75** 12 k Ω ; 9.05 MHz, 101 MHz, 74.8 MHz, 320 MHz; 2.60 MHz, 44.6 pF
- 18.77** (a) 81.9°
- 18.79** 6.32 pF; 315 MHz, 91.5 MHz; 89.4°
- 18.81** 17.5 MHz; [20.1 MHz, 36.3 MHz]; 0.211 mS, 5.28 μ A
- 18.82** 5.17 MHz, 4.53 MHz
- 18.84** 9.00 MHz, 1.20
- 18.86** 7.96 MHz, 8.11 MHz, 1.05
- 18.88** 7.5 MHz, 80 V_{p-p}
- 18.89** 7.96 MHz
- 18.90** 11.1 MHz, 18.1 MHz, 1.00
- 18.91** $L_{EQ} = L_1 + L_2$ | $R_{EQ} = -\omega^2 g_m L_1 L_2$
- 18.92** $\omega_o^2 = \frac{1}{L(C + C_{GS} + 4C_{GD})}$ | $\mu_f \geq 1 + \frac{r_o}{R_p}$
- 18.94** 5.13 pF; 1 GHz can't be achieved.
- 18.95** 6.33 pF; 2.81 mA; 3.08 mA; 1.32 V
- 18.97** 15.915 mH, 15.915 fF; 10.008 MHz, 10.003 MHz
- 18.99** 9.28 MHz; 9.19 MHz